



C09-M-304/CHST-304

3248

BOARD DIPLOMA EXAMINATION, (C-09)

MARCH/APRIL—2018

DME—THIRD SEMESTER EXAMINATION

ELECTRICAL ENGINEERING AND BASIC ELECTRONICS

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

- Instructions** : (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Define work, power and energy and mention their units.
2. Define (a) self-inductance and (b) mutual inductance.
3. State Faraday's laws of electromagnetic induction.
4. State the materials used for the following parts of DC generators :
 - (a) Yoke
 - (b) Armature core
 - (c) Brushes
5. State the applications of DC series motor.
6. State the relation between frequency and speed of an alternator.

/3248

1

[Contd...

WWW.MANARESULTS.CO.IN

7. Define (a) ^{*}amplitude, (b) time period and (c) frequency.
8. Define capacity of battery.
9. Briefly explain the formation of *P-N* junction diode.
10. State the procedure to be immediately adopted in case of electric shocks.

PART—B

10×5=50

Instructions : (1) Answer *any five* questions.
(2) Each question carries **ten** marks.
(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. A house has the following loads :

- (a) 10 lamps of 60 W each working for 8 hours a day
- (b) 4 lamps of 100 W each working for 5 hours a day
- (c) 2 heaters of 1000 W each working for 3 hours a day
- (d) 5 fans of 100 W each working for 12 hours a day

Calculate the total number of units consumed in 30 days and the amount of bill at the rate of 50 paisa/unit.

12. (a) A resistor of 4 ohms is connected in parallel to the resistor of 8 ohms and the whole combination is connected in series with a resistor of 2 ohms. Calculate the effective resistance.

^{*} (b) Classify DC generators on the basis of excitation.

13. (a) Explain the working principle of DC motor.

(b) A 250 V DC motor takes 41 A at full load. Its armature and shunt field resistance are 0.1 ohm and 250 ohms. Find back e.m.f on full load.

14. A series circuit having a resistance of 40 ohms, capacitance of 20 micro Faradays and inductance of 0.2 H is connected across 110 V, 50 Hz supply. Calculate (a) impedance, (b) current and (c) power factor.

15. Explain the ^{*} star-delta starter of three-phase induction motor with a neat sketch.
16. (a) A 1-phase 210 V, 50 Hz supply is connected across a series circuit consisting of 6 ohms resistance and an unknown inductance. Find the inductance if the current drawn from the supply is 10 A.
- (b) Explain the construction of lead acid cell.
17. Explain the working of *N-P-N* transistor with a neat sketch.
18. Explain the construction and working principle of moving coil voltmeter.
