

III B. Tech I Semester Supplementary Examinations, March- 2021
PULSE AND DIGITAL CIRCUITS
 (Common to Electronics and Communication Engineering, Electronics and
 Instrumentation Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answering the question in **Part-A** is compulsory
 3. Answer any **THREE** Questions from **Part-B**

PART -A

(22 Marks)

1. a) Draw the response of high pass RC circuit for a ramp input. [4M]
- b) Draw the basic circuit diagram of negative peak clamper circuit. [3M]
- c) When transistor acts as a switch? Explain. [4M]
- d) Compare different types of multivibrators. [4M]
- e) Write the Methods of Generating Time Base Waveform. [4M]
- f) Compare unidirectional and bi-directional Sampling Gates. [3M]

PART -B

(48 Marks)

2. a) Prove that for any periodic input waveform the average level of the steady state output signal from the RC high pass circuit is always zero. [8M]
- b) Draw the output of the high pass RC circuit for square wave input. Derive the expression for percentage tilt for a square wave output of RC high pass circuit. [8M]
3. a) With the help of a neat circuit diagram explain the working of a two-level diode clipper. [8M]
- b) What is a comparator? List out the applications of a voltage comparator. [8M]
4. a) Design a TTL NAND gate and explain the operation with the help of function table. [8M]
- b) For a CE circuit $V_{CC} = 10V$, $R_C = 1K$, $I_B = 0.2A$. Determine: [8M]
 - i) The value of $h_{fe}(\min)$ for saturation to occur,
 - ii) If R_C is change to 220Ω , will the transistor be saturated?
5. a) Draw and explain the working principle of astable multivibrator circuit and also explain the merits and limitations of it. [8M]
- b) With the help of a neat circuit diagram and waveform, explain the principle of operation of collector coupled monostable multivibrator. [8M]
6. Explain the following methods of linearizing a voltage sweep with a neat diagram: [16M]
 - i) Miller Sweep
 - ii) Bootstrap sweep.
 Compare their merits and limitations.
7. a) Discuss in detail the sine wave frequency division with a sweep circuit. [8M]
- b) What is phase jitter? How to reduce it in frequency division? [8M]
