

III B. Tech I Semester Supplementary Examinations, May - 2016
PULSE AND DIGITAL CIRCUITS
 (Common to ECE and EIE)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answering the question in **Part-A** is compulsory
 3. Answer any **THREE** Questions from **Part-B**

PART -A

- | | | |
|---|---|------|
| 1 | a) Describe about ringing circuit. | [3M] |
| | b) State clamping circuit theorem. | [4M] |
| | c) Explain piecewise linear characteristics of a diode. | [4M] |
| | d) What are the types of triggering? Distinguish between them. | [4M] |
| | e) What are the applications of Time-base generator? | [3M] |
| | f) What do you mean by sampling gate? Give the applications of sampling gate? | [4M] |

PART -B

- | | | |
|---|--|------|
| 2 | a) Discuss about attenuators. | [4M] |
| | b) Analyze the low pass circuit for the exponential inputs, with help of waveforms. | [8M] |
| | c) Discuss the application of an attenuator in a CRO. | [4M] |
| 3 | a) Draw the basic circuit diagram of positive peak clamper circuit and explain its operation. | [8M] |
| | b) Explain transfer characteristics of emitter coupled clipper and derive necessary equations. | [8M] |
| 4 | a) Draw the circuits of 3-input OR-gate using diodes for:
(i) Positive logic, (ii) Negative logic and explain the operation of circuit. | [8M] |
| | b) Give the comparison of different logic families. | [8M] |
| 5 | a) What are different types of multivibrators? Explain the stable state of a multivibrator. | [8M] |
| | b) Sketch the circuit diagram of Schmitt trigger and explain its operation. | [8M] |
| 6 | a) With the help of neat circuit diagram and waveforms explain transistor miller time base generator. | [8M] |
| | b) Discuss about the recovery time of a sweep circuit. How do you achieve short recovery time? | [8M] |
| 7 | a) Explain the process of synchronization of a sweep circuit. | [8M] |
| | b) Write notes on:
i) Astable relaxation circuits ii) Monostable relaxation circuits | [8M] |
