

**III B. Tech I Semester Supplementary Examinations, August - 2021****PULSE AND DIGITAL CIRCUITS**

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)2. Answering the question in **Part-A** is compulsory3. Answer any **THREE** Questions from **Part-B**

\*\*\*\*\*

**PART -A****(22 Marks)**

1. a) Sketch the response of RC Low pass when square wave as input  $t \approx T_p$ . [4M]
- b) Classify the clippers. [4M]
- c) Define  $T_{on}$  and  $T_{off}$  of a Transistor Switching time. [3M]
- d) Classify and define Multivibrators. [3M]
- e) If Transmission error is 8 ms, estimate the Sweep speed error and displacement error. [4M]
- f) Explain the need of Synchronization and frequency division. [4M]

**PART -B****(48 Marks)**

2. a) Derive the response of RC low pass circuit when the sinusoidal signal is given as input. [8M]
- b) Explain the operation of RC double differentiator circuit. [8M]
3. a) Explain the function of basic parallel Clipper circuit during positive and negative periods of Sinusoidal signal. [8M]
- b) Explain the function of Voltage Comparator Circuit. [8M]
4. a) Explain the working principle of Monostable Mutivibrator with wave forms. [8M]
- b) Determine the period and frequency of oscillation for an astable multivibrator component values  $R_1= 2 \text{ k}\Omega$ ,  $R_2=10 \text{ k}\Omega$ ,  $C_1=0.01 \text{ }\mu\text{F}$  and  $C_2=0.05 \text{ }\mu\text{F}$ . [8M]
5. a) Explain piece-wise linear diode characteristics. [8M]
- b) Design 2 i/p AND gate using DTL and explain its operation. [8M]
6. a) Draw the circuit diagram of a transistor miller - time base generator and explain its working. [8M]
- b) Define the sweep speed error, displacement error and transmission error of voltage time-base waveform. [8M]
7. a) Explain the principle of synchronization. [8M]
- b) Compare the unidirectional and bidirectional sampling gates with suitable diagrams. [8M]

\*\*\*\*\*