

III B.Tech I Semester Supplementary Examinations, October/November - 2019
PULSE AND DIGITAL CIRCUITS

(Common to Electronics and Communication Engineering, Electronics and
Instrumentation Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answering the question in **Part-A** is compulsory
 3. Answer any **THREE** Questions from **Part-B**

PART -A

(22 Marks)

- | | | |
|------|--|------|
| 1 a) | Define Linear Wave Shaping. | [4M] |
| b) | Justify that a clamping circuit is a dc inserter. | [3M] |
| c) | Define rise time and transition time of a diode. | [4M] |
| d) | What is hysteresis? how it can be eliminated in a Schmitt trigger? | [3M] |
| e) | What are the general features of a time base signal? | [4M] |
| f) | Name some negative resistance devices used as relaxation Oscillator. | [4M] |

PART -B

(48 Marks)

- | | | |
|------|--|------|
| 2 a) | Explain the operation of attenuators. | [5M] |
| b) | A symmetrical square wave of peak to peak amplitude V and frequency f is applied to a high pass RC circuit. Find the percentage tilt. | [8M] |
| c) | What is Ringing circuit? | [3M] |
| 3 a) | Explain transfer characteristics of the emitter coupled clipper. | [4M] |
| b) | Draw the basic circuit diagram of positive peak clamper circuit and explain its operation. | [8M] |
| c) | What do you mean by compensation? Explain in detail. | [4M] |
| 4 a) | What are the saturation parameters of transistor and explain their variation with respect to temperature. | [8M] |
| b) | Derive expressions for rise time and fall time in terms of the transistor parameters and operating currents. | [8M] |
| 5 a) | Explain the principle of operation of Monostable multivibrators. | [8M] |
| b) | Design a collector coupled Mono-stable for the following specifications: I_{CBO} and voltage drops across saturated transistors are negligible. For the transistors $h_{FE (min)}=20$, and the base-emitter cutoff voltage for the normally OFF transistor is -1 V. The base drive to the transistor in saturation is 50% in excess of minimum required. Collector supply voltage is 6V and collector current=2 mA the delay time is 3000 μ sec. Choose $R_1=R_2$. Find R_C , R , R_1 , C and V_{BB} . | [8M] |
| 6 a) | Define and derive the terms slope error, displacement error and transmission error. | [8M] |
| b) | Explain the working of a Miller sweep circuit and derive expression for the slope sweep error. | [8M] |
| 7 a) | With a neat circuit, explain a method of compensation used to improve the linearity of a bootstrap time base circuit. | [8M] |
| b) | Explain the principle of "synchronization" and synchronization with frequency division. | [8M] |
