

**III B.Tech I Semester Supplementary Examinations, October/November - 2019**  
**PULSE AND DIGITAL CIRCUITS**

(Common to Electronics and Communication Engineering, Electronics and  
Instrumentation Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)  
 2. Answering the question in **Part-A** is compulsory  
 3. Answer any **THREE** Questions from **Part-B**

**PART -A**

(22 Marks)

- 1 a) Define Linear Wave Shaping. [4M]
- b) Justify that a clamping circuit is a dc inserter. [3M]
- c) Define rise time and transition time of a diode. [4M]
- d) What is hysteresis? how it can be eliminated in a Schmitt trigger? [3M]
- e) What are the general features of a time base signal? [4M]
- f) Name some negative resistance devices used as relaxation Oscillator. [4M]

**PART -B**

(48 Marks)

- 2 a) Explain the operation of attenuators. [5M]
- b) A symmetrical square wave of peak to peak amplitude  $V$  and frequency  $f$  is applied to a high pass RC circuit. Find the percentage tilt. [8M]
- c) What is Ringing circuit? [3M]
- 3 a) Explain transfer characteristics of the emitter coupled clipper. [4M]
- b) Draw the basic circuit diagram of positive peak clamper circuit and explain its operation. [8M]
- c) What do you mean by compensation? Explain in detail. [4M]
- 4 a) What are the saturation parameters of transistor and explain their variation with respect to temperature. [8M]
- b) Derive expressions for rise time and fall time in terms of the transistor parameters and operating currents. [8M]
- 5 a) Explain the principle of operation of Monostable multivibrators. [8M]
- b) Design a collector coupled Mono-stable for the following specifications:  $I_{CBO}$  and voltage drops across saturated transistors are negligible. For the transistors  $h_{FE (min)}=20$ , and the base-emitter cutoff voltage for the normally OFF transistor is  $-1$  V. The base drive to the transistor in saturation is 50% in excess of minimum required. Collector supply voltage is 6V and collector current=2 mA the delay time is 3000  $\mu$ sec. Choose  $R_1=R_2$ . Find  $R_C$ ,  $R$ ,  $R_1$ ,  $C$  and  $V_{BB}$ . [8M]
- 6 a) Define and derive the terms slope error, displacement error and transmission error. [8M]
- b) Explain the working of a Miller sweep circuit and derive expression for the slope sweep error. [8M]
- 7 a) With a neat circuit, explain a method of compensation used to improve the linearity of a bootstrap time base circuit. [8M]
- b) Explain the principle of "synchronization" and synchronization with frequency division. [8M]

\*\*\*\*\*