

**III B. Tech I Semester Supplementary Examinations, May - 2018****LINEAR IC APPLICATIONS**

(Common to Electronics and Communication Engineering, Electronics and Instrumentation Engineering and Electronics and Computer Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)  
 2. Answering the question in **Part-A** is compulsory  
 3. Answer any **THREE** Questions from **Part-B**

**PART -A**

- |   |    |  |      |
|---|----|--|------|
| 1 | a) | What are the properties of dual input unbalanced output differential amplifier?          | [3M] |
|   | b) | Define CMRR of op-amp.   | [3M] |
|   | c) | Derive the gain of non inverting amplifier.  | [4M] |
|   | d) | Draw the schematic of a second order High-pass filter and sketch the frequency response. | [4M] |
|   | e) | Mention the applications of 555 timer used as Monostable and Astable operations.         | [4M] |
|   | f) | What are the specifications of AD 574 (12 bit ADC)                                       | [4M] |

**PART -B**

- |   |    |  |       |
|---|----|--|-------|
| 2 | a) | Analyze the dual input balanced output configuration of differential amplifier using DC.                                   | [8M]  |
|   | b) | Write and Explain about DC coupling and cascaded differential amplifier stages.  | [8M]  |
| 3 | a) | Briefly explain the various types of IC packages. Mention the criteria for selecting an IC package.                        | [8M]  |
|   | b) | With a neat sketch explain the frequency compensation using pole – zero method.  | [8M]  |
| 4 | a) | Explain, how to obtain triangular wave using a square wave generator.  | [8M]  |
|   | b) | Draw the circuit of Log and Anti log Amplifiers explain its operation.   | [8M]  |
| 5 | a) | Compare Active filters with passive filters.   | [6M]  |
|   | b) | Discuss in detail about band pass and band reject filters.   | [10M] |
| 6 | a) | Explain the operation of astable multivibrator using 555 IC Timer.   | [8M]  |
|   | b) | Design a Mono stable multivibrator for 3ms pulse width.  | [8M]  |
| 7 | a) | Draw the circuit of weighted resistor DAC and derive expression for output analog voltage $V_o$ .                          | [10M] |
|   | b) | Find out step size and analog output for 4 -bit R-2R ladder DAC, when input is 0 1 1 1 and 1 1 1 1, assume $V_{ref}=+5V$ . | [6M]  |

\*\*\*\*\*

