

Code No: **RT31042**

**R13**

SET - 1

**III B. Tech I Semester Supplementary Examinations, August -2021**  
**LINEAR IC APPLICATIONS**

(Common to Electronics and Communication Engineering, Electronics and Instrumentation Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)  
2. Answering the question in **Part-A** is compulsory  
3. Answer any **THREE** Questions from **Part-B**

\*\*\*\*\*

**PART -A**

**(22 Marks)**

1. a) Write the ideal characteristics of an operational amplifier. [3M]
- b) Describe different package types of op-amps. [4M]
- c) List out the applications of V-I and I-V converters. [4M]
- d) Draw the circuit diagram of op-amp all pass filter. [4M]
- e) Write the various applications of VCO 566. [4M]
- f) Define accuracy and resolution of the digital-to-analog converters. [3M]

**PART -B**

**(48 Marks)**

2. a) Derive an expression for voltage gain for dual input balanced output differential amplifier. [8M]
- b) Explain the operation of level translator with the help of a neat circuit diagram. [8M]
3. a) With suitable sketches, explain the measurement procedure for the slew rate. [8M]
- b) An op-amp has a slew rate of  $3 \text{ V}/\mu\text{s}$ . What is the maximum frequency of an output sinusoid of peak value  $5 \text{ V}$  at which the distortion sets in due to the slew rate limitation? [8M]
4. a) Explain the operation of a square wave generator using op-amp with a neat circuit diagram. [8M]
- b) What is the output voltage of integrator when step input voltage of  $5 \text{ V}$  with  $5 \text{ ms}$  is applied to the circuit. [8M]
5. a) Explain the operation of IC 1496 balanced modulator with a neat sketch. [8M]
- b) Explain the operation of 2<sup>nd</sup> order band pass filter with a neat diagram. [8M]
6. a) Design a symmetrical square wave generator with  $4\text{V}$  peak value and  $2 \text{ KHz}$  frequency using 555 timer. Assume necessary data. [8M]
- b) Draw the circuit diagram of monostable multivibrator by using 555 IC timer and explain its operation. [8M]
7. a) Explain the operation of dual slope ADC with a neat circuit diagram. [8M]
- b) Describe the advantages and disadvantages of flash type ADC. [8M]

\*\*\*\*\*