

III B. Tech I Semester Supplementary Examinations, May – 2016
DIGITAL SYSTEM DESIGN & DIGITAL IC APPLICATIONS
(Common to ECE and EIE)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
2. Answering the question in **Part-A** is compulsory
3. Answer any **THREE** Questions from **Part-B**

PART -A

- 1 a) What are the steps involved in FPGA Design Flow using VHDL. [4M]
b) Define simulation and synthesis. [4M]
c) Write the advantages of PLA over other simple PLDs. [4M]
d) Draw the CMOS inverter circuit and Explain. [3M]
e) Write VHDL code for half subtractor using data flow modeling. [4M]
f) Write VHDL code for D Flip Flop with asynchronous reset using behavioral modeling. [3M]

PART -B

- 2 a) Explain the data types in VHDL. [5M]
b) Write in brief about the history of VHDL. [5M]
c) What are the different types of objects in VHDL? Explain. [6M]
- 3 a) What is the importance of constraints in VHDL? Explain various constraints. [8M]
b) Explain Electronic Design Interchange Format netlist representation in detail. [8M]
- 4 a) Draw and explain the 1-bit memory cell of a Dynamic RAM. [8M]
b) Implement a 2-bit squarer logic circuit using PROM. [8M]
- 5 a) What is the necessity of interfacing in logic circuits? Write a brief note on interfacing TTL with CMOS? [8M]
b) Draw and explain the 2-input NAND gate using TTL logic. [8M]
- 6 a) Explain the operation of 8-bit barrel shifter with a neat diagram. [8M]
b) Write VHDL codes which convert a fixed point number into a floating point number. [8M]
- 7 a) Write VHDL code for a 3-bit synchronous binary even counter. [8M]
b) Design MOD-16 synchronous counter using T- Flip-Flop? [8M]
