

III B. Tech I Semester Supplementary Examinations, October/November- 2019
DIGITAL SYSTEM DESIGN & DIGITAL IC APPLICATIONS

(Common to Electronics and Communication Engineering, Electronics and
Instrumentation Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answering the question in **Part-A** is compulsory
 3. Answer any **THREE** Questions from **Part-B**

PART -A

(22 Marks)

1. a) What do you mean by concurrent statement? [4M]
- b) What is net list? [3M]
- c) Explain the 2D decoding technique. [4M]
- d) State the noise margin for CMOS family. [3M]
- e) Briefly discuss about priority encoder. [4M]
- f) List out the differences between asynchronous and synchronous counter. [4M]

PART -B

(48 Marks)

2. a) With the help of block diagram, explain the program structure of VHDL. [8M]
- b) List out the differences between various VHDL functions and procedures with example. [8M]
3. a) Explain the synthesis process with suitable a block diagram. [8M]
- b) Explain how a logic level simulation can verify complex circuits compared to other simulations? [8M]
4. a) Explain the internal structure of 64Kx1 DRAM with the help of timing waveforms. [8M]
- b) Discuss how PROM, EPROM and EEPROM technologies different from each other? [8M]
5. a) Draw the circuit diagram and functional table of ECL 10K 2-input OR/NOR gate and explain its operation. [8M]
- b) Which bipolar family is best suited for LSI? Draw the circuit of a 4-input NAND gate using CMOS transistors. [8M]
6. a) Using a process statement write a VHDL source code for 4 to 1 multiplexer. [8M]
- b) Design a function $F = ABC + (A+B+C)'$ by using IC 74X138. [8M]
7. a) Discuss the logic circuit of IC 74x377 register. Write a VHDL program for the same in structural style. [8M]
- b) Draw the logic diagram of 74x74 IC and explain the operation. Develop the VHDL model for this IC. [8M]
