

3235

BOARD DIPLOMA EXAMINATION, (C-09) OCT / NOV-2015

DECE - THIRD SEMESTER EXAMINATION FLECTRONIC CIRCLITS I

Time: 3 hours [Total Marks: 80

PART - A

 $3 \times 10 = 30$

Instructions: (1) Answer all questions

- (2) Each questions carries three marks
- (3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.
- 1. Draw the circuit of full-wave centre-tapped rectifier
- 2. Draw the block diagram of on-line UPS
- 3. Define voltage regulation.
- 4. Define gain, frequency response and bandwidth of an amplifier
- 5. Explain the need for proper biasing in amplifier circuits.
- **6.** Draw the hybrid equivalent of a transistor in CE mode.
- 7. Define the parameters of JFET.
- 8. Draw the equivalent circuit of UJT.
- 9. List different IC packages.
- 10. State the advantages of ICs over discrete assembly.

/**3235** [Contd...

PART - B $10 \times 5 = 50$

Instructions: (1) Answer any five questions.

- (2) Each question carries ten marks.
- (3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.
- 11. (a) Compare half-wave, centre-tapped, full-wave and bridge rectifier.
 - (b) Explain the need for a filter in power supplies and list different types of filters.
- **12.** Derive expressions for RMS value, average value, Ripple factor and efficiency of a half-wave rectifier.
- 13. Draw the circuit diagram of Darlington pair and explain its working briefly. List any four applications.
- **14.** Explain the selection of operating point on the DC load line with wave forms.
- **15.** Explain the construction and principle of operation of enhancement type of *n*-channel MOSFET.
- **16.** (a) Explain the principle of operation of CMOSFET.
 - (b) Explain the principle of working of Varactor Diode and draw its characteristic.
- **17.** Draw the block diagram and the pin out diagram of IC 741 and explain each block and each pin briefly.
- **18.** (a) Draw and explain the differential amplifier circuit.
 - (b) Draw and explain the Op-Amp Summing Amplifier

* * *

/3235 2 AA15–PDF

WWW.MANARESULTS.CO.IN