



C09-EC-303

**3235**

**BOARD DIPLOMA EXAMINATION, (C-09)  
OCT/NOV—2017  
DECE—THIRD SEMESTER EXAMINATION  
ELECTRONIC CIRCUITS—I**

*Time : 3 hours ]*

*[ Total Marks : 80*

---

**PART—A**

3×10=30

**Instructions :** (1) Answer **all** questions.  
(2) Each question carries **three** marks.  
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Draw the block diagram of OFF-line UPS.
2. List different types of filters.
3. Draw the circuit diagram of a half-wave rectifier.
4. Define  $h$  parameters of a transistor.
5. State the need for multistage amplifiers.
6. Classify the amplifiers based on period of conduction of collector current.
7. Compare JFET and MOSFET.
8. List the applications of FETs.

/3235

1

[ *Contd...*

[www.ManaResults.co.in](http://www.ManaResults.co.in)

9. List the <sup>\*</sup>advantages of surface-mount technology (SMT) over pin through hole (PTH) mounting.
10. Classify ICs based on manufacturing process.

**PART—B**

10×5=50

**Instructions :** (1) Answer *any five* questions.  
(2) Each question carries **ten** marks.  
(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. Draw and explain the working of bridge rectifier with waveforms. 3+5+2
12. (a) Explain the operation of transistor series voltage regulator. 7  
(b) List the types of IC regulators. 3
13. Explain collector to base resistor method of biasing and list its advantages and disadvantages. 6+2+2
14. Explain the principle of operation of two-stage transformer coupled amplifier with circuit diagram and draw its frequency response. 3+5+2
15. Explain the construction and principle of operation of enhancement-type *n*-channel MOSFET. 4+6
- \* 16. Explain the construction and principle of operation of *n*-channel JFET, and also draw its drain characteristics. 4+4+2
17. Draw the block diagram of IC 741 and explain each block. 3+7
18. Explain the fabrication of resistor and capacitor on monolithic IC. 5+5

\*\*\*