



C09-EC-306

3238

**BOARD DIPLOMA EXAMINATION, (C-09)
MARCH/APRIL—2016
DECE—THIRD SEMESTER EXAMINATION**

CIRCUIT THEORY

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

- Instructions :** (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Differentiate between AC and DC.
2. Define active and passive elements and give examples.
3. Define quality factor in resonance circuit.
4. Write the formula for star-to-delta transformation.
5. Define (a) branch, (b) node, and (c) loop.
6. Write the limitations of Thevenin's theorem.
7. State superposition theorem.
8. Define steady-state and transient response.
9. Draw a circuit of high-pass and low-pass RC circuit.
10. Define linear wave shaping.

/3238

1

[Contd...

WWW.MANARESULTS.CO.IN

*

PART—B

10×5=50

- Instructions :** (1) Answer *any five* questions.
(2) Each question carries **ten** marks.
(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. (a) Derive the expression for alternating current through series RC circuit and obtain $V-I$ relation. 5

(b) A capacitor having $C = 10 \mu\text{f}$ is connected in series with a resistance of 120Ω across 100-V, 50-Hz supply. Calculate current, phase angle and power consumed. 5

12. (a) Distinguish between series and parallel resonance circuits. 4

(b) A series circuit $R = 5 \Omega$, $L = 20 \text{ mH}$ and a variable capacitance C has an applied voltage with a frequency $f = 1000 \text{ Hz}$. Find the capacitance for series resonance. 3

(c) Define half-power frequencies. 3

13. (a) Define the driving-point impedance and transfer impedance. 4

*

(b) For the network shown in Fig. 1 below, calculate the currents I_1 and I_2 using mesh analysis : 6

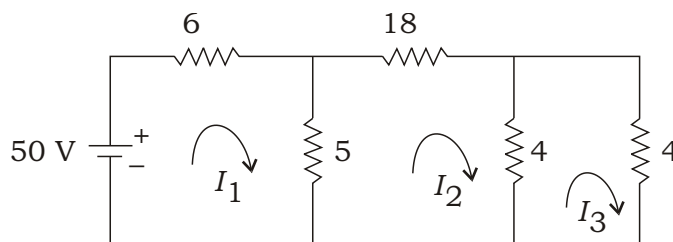


Fig. : 1

14. (a) For the network shown in Fig. 2 below, find the voltage transfer function V_o/V_i by using Nodal method : 6

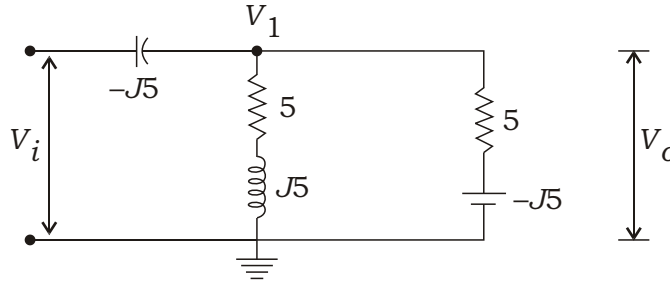


Fig. 2

- (b) State Kirchhoff's current law and voltage law. 4
15. (a) State Norton's theorem and give its limitations. 4
- (b) Find the current in $(2 - j3)$ branch for the network shown in Fig. 3 below using superposition theorem : 6

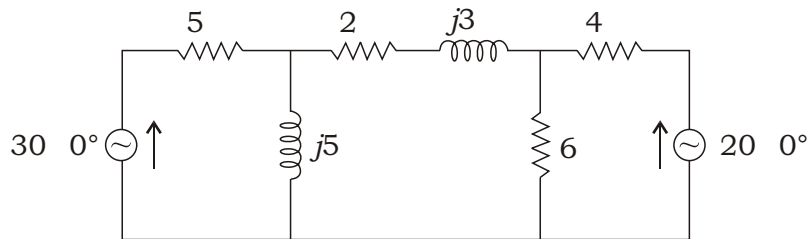


Fig. 3

16. (a) State the maximum power transfer theorem for DC network. 3
- (b) Define the reciprocity theorem and give its limitations. 4
- (c) Explain ideal current source and ideal voltage source briefly. 3
17. (a) Derive the relation among L_1 , L_2 , M and K . 5
- (b) Two identical coils with $L = 0.02$ H have a $K = 0.08$. Find two equivalent inductances with the coils connected in series aiding and series opposing. 5
18. (a) Explain how a low-pass RC circuit works as an integrator. 5
- (b) Mention the application of a high-pass and a low-pass RC circuit. 5
