



C09-EC-306

3238

**BOARD DIPLOMA EXAMINATION, (C-09)
OCT/NOV—2018
DECE—THIRD SEMESTER EXAMINATION**

CIRCUIT THEORY

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

- Instructions** : (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Distinguish between a.c. and d.c.
2. Define bandwidth and selectivity of a resonant circuit.
3. State the phase relationship between voltage and current for the following components :
 - (a) Resistor
 - (b) Capacitor
 - (c) Inductor
4. Define driving point impedance and transfer impedance.

/3238

1

[Contd...

WWW.MANARESULTS.CO.IN

5. State Kirchhoff's current law and voltage law.
6. Define superposition theorem.
7. Define Norton's theorem.
8. Draw a high pass R - C circuit.
9. Define time constant of series R - C circuit.
10. Two coils connected in series having an equivalent inductance of 0.8 H when connected in aiding and equivalent inductance of 0.5 H when connected in opposing. Calculate the mutual inductance of the coils.

PART—B

10×5=50

Instructions : (1) Answer *any five* questions.


(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. (a) Distinguish between series resonance and parallel resonance. 4
- (b) Derive the expression for the resonant frequency of a series R - L - C circuit and write the expressions for current and impedance at resonance. 6
12. A capacitor having a capacitance of 10 μ F is connected in series with a pure resistance of 120 Ω across a 100-V, 50-Hz supply. Calculate (a) current I , (b) phase angle ϕ , and (c) power consumed.


13. (a) Find the voltage transfer function V_o / V_i for the circuit shown below, using mesh current analysis :

6

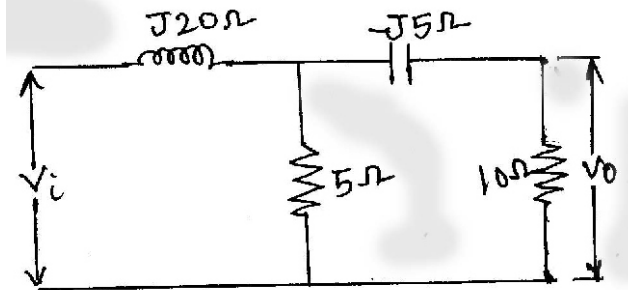


- (b) Obtain the star equivalent circuit for the delta connected circuit shown below :

4

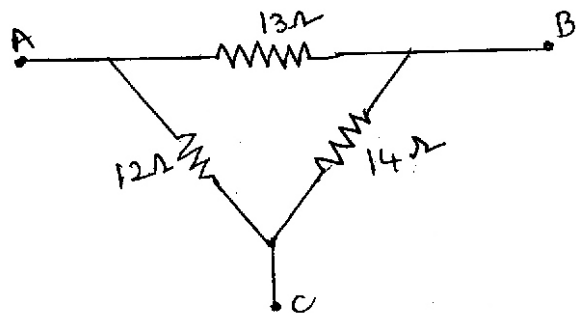

14. (a) Determine the voltage at nodes 1 and 2 of the network shown below by using nodal analysis :

6

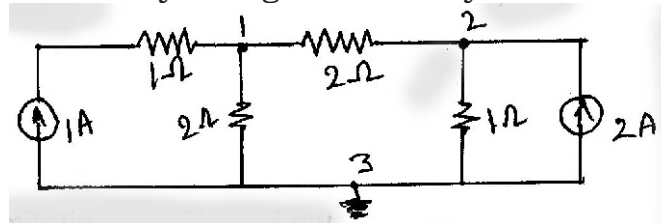


- (b) Write the limitations of Ohm's law.


4

15. Obtain Thevenin's equivalent circuit for the circuit shown below at terminals A and B :


10

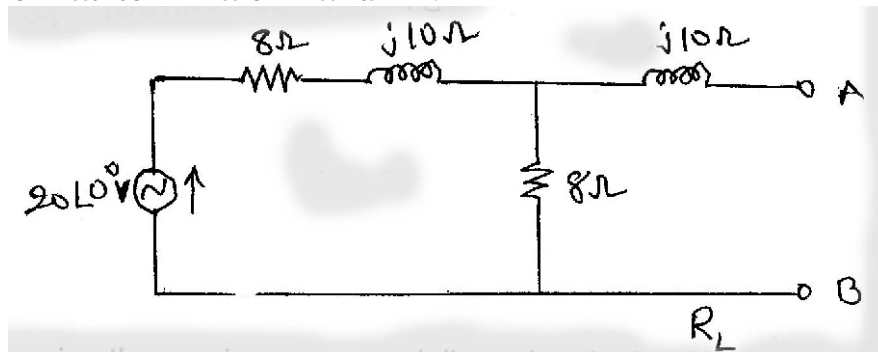

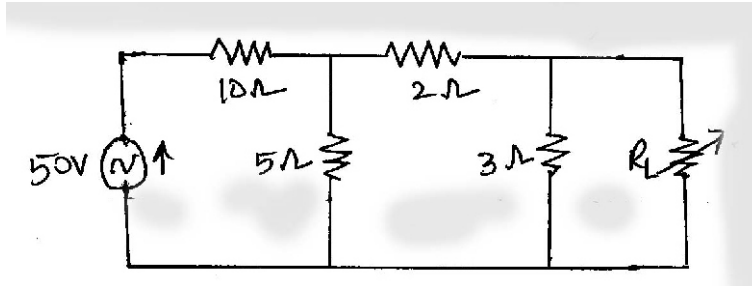16. Determine the maximum power delivered to the load R_L in the circuit shown below : 10



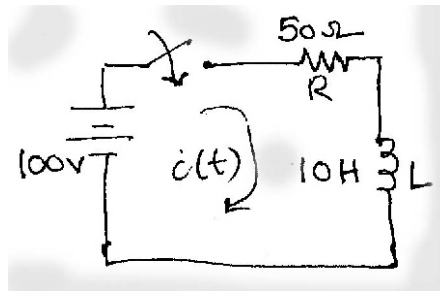17. (a) A series R - L circuit with $R = 50 \Omega$ and $L = 10 \text{ H}$ has a constant voltage $V = 100 \text{ volts}$ applied at $t = 0$ by closing a switch. Find the expression for current $i(t)$: 5



- (b) Draw the response of a low-pass R - C circuit for a square wave input with different time constants. 5
18. (a) Explain that a high-pass R - C circuit works as a differentiator. 5
- (b) Explain the reflected impedance significance in coupled circuit and give the expression for the reflected impedance. 5
