\* 3 7 6 1 \*

со9-ес-605

## 3761

## BOARD DIPLOMA EXAMINATION, (C-09) MARCH/APRIL—2017 DECE—SIXTH SEMESTER EXAMINATION

## INDUSTRIAL ELECTRONICS

Time : 3 hours ]

\*

[ Total Marks : 80

		PART—A	3×10=30
Inst	ructio	ons: (1) Answer <b>all</b> questions. (2) Each question carries <b>three</b> marks.	
		<ul><li>(3) Answers should be brief and straight to the shall not exceed <i>five</i> simple sentences.</li></ul>	point and
1.	Sket	ch the ISI symbols for SUS, SBS, SCS.	1+1+1=3
2.	Give	the different triggering modes of TRIAC.	3
3.	Give	the definition of transducer.	3
4.	Expl	ain the principle of thermocouple.	3
5.	List	the applications of AC regulator.	3
6.	Ment	tion the methods to control the speed of AC motor	. 3
7.	List	the applications of inverter.	3
8.	Give	some examples of active transducers.	3
/3761		1 WWW.MANARESULTS.CO.IN	[ Contd

- **9.** Draw the two transistor model of SCR. 3
- **10.** List the methods of generating ultrasonic waves. 3

Instructions : (1) Answer any five questions.

- (2) Each question carries **ten** marks.
- (3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11.	Explain the working of SMPS with block diagram.	5+5=10
12.	(a) Explain the working LASCR.	4
	(b) Explain the working of IGBT.	6
13.	Draw and explain the working of three phase fully contro converter with resistive load.	olled 5+5=10

- **14.** Explain the operation of chopper in all four quadrants. 10
- **15.** Explain the construction and working of LVDT. 10
- **16.** Explain the working of single-phase full-bridge inverter. 10
- 17. Draw and explain the working of pulsed echo ultrasonic flow detector. 5+5=10
- 18. Explain the working principle, construction and working of Piezo-electric transducer. 3+3+4=10

/3761 2 AA7(A)—PDF WWW.MANARESULTS.CO.IN