



C09-EE-303

3241

BOARD DIPLOMA EXAMINATION, (C-09)

MARCH/APRIL—2017

DEEE—THIRD SEMESTER EXAMINATION

ELECTRICAL CIRCUITS

Time : 3 hours ]

[ Total Marks : 80

PART—A

3×10=30

**Instructions** : (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answer should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Define active circuit and passive circuit.
2. State Thevenin's theorem.
3. Define average value, form factor and peak factor.
4. Derive the RMS value of a full-wave rectified sine waveform.
5. Perform and represent in polar form (a)  $A = 5 + j6$  and (b)  $A / B$ , where  $A = 5 + j6$  and  $B = 6 + j8$ .
6. Derive an expression for current in pure capacitive circuit, when an alternating voltage  $v = V_m \sin t$  is applied.
7. State the formula for power factor in  $R-L-C$  series circuit.
8. Compare series with parallel resonant circuits.

/3241

1

[ Contd...

WWW.MANARESULTS.CO.IN

9. Give the advantage of polyphase system.
10. List the relation between line values and phase values in star and delta connected systems.

**PART—B**

10×5=50

- Instructions :** (1) Answer any **five** questions.  
 (2) Each question carries **ten** marks.  
 (3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. (a) State Kirchoff's laws. 4  
 (b) Determine the equivalent resistance across AB of the circuit shown in Fig. 1 : 6

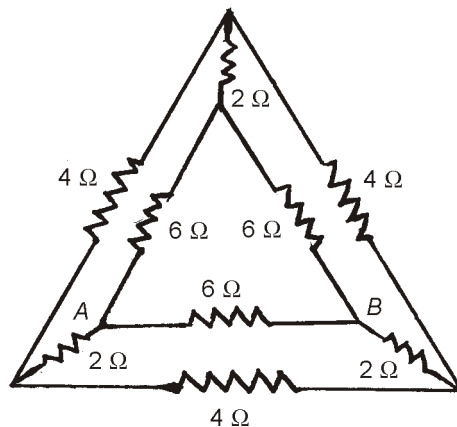


Fig. 1

12. Find the current through 20 resistance of the network (Fig. 2) by using superposition theorem : 10

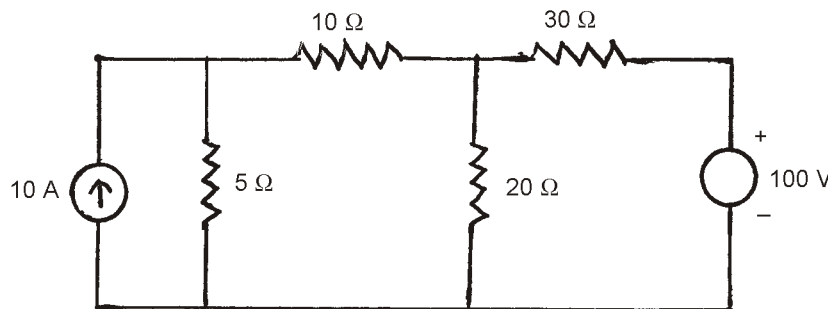


Fig. 2

13. (a) State and explain the maximum power transfer theorem. 7
- (b) The equation of an alternating current is  $i = 100 \sin 628t$ . Determine—
- (i) RMS value;
- (ii) average value;
- (iii) time period. 3
14. (a) Convert the following rectangular to polar or polar to rectangular : 4
- (i)  $4 - j6$
- (ii)  $20 \angle 30^\circ$
- (b) Show the average power consumed in an inductor and a capacitor is zero. 6
15. A resistance of  $10 \Omega$  and inductance of  $0.1 \text{ H}$  are connected in series across a supply of  $220 \text{ V}$  and  $50 \text{ Hz}$ . Determine (i) the impedance, (ii) current flowing, (iii) power factor, (iv) the phase angle between  $V$  and  $I$  and (v) total power consumed. 10
16. Two impedances  $Z_1 = 10 - j15 \Omega$  and  $Z_2 = 6 + j8 \Omega$  are connected in parallel. If the total current supplied is  $15 \text{ A}$ , find the voltage applied, current and the power taken by each branch. 10
17. A series RLC circuit consists of  $1000 \Omega$ ,  $L = 100 \text{ mH}$  and  $C = 10 \text{ pF}$ . If the applied voltage across the circuit is  $100 \text{ V}$ , find (a) resonant frequency, (b) current at resonance and (c)  $Q$ -factor of the circuit. 10
18. A balance 3- star connected load of  $150 \text{ kW}$  takes a leading current of  $100 \text{ A}$  with a line voltage of  $1100 \text{ V}$  at  $50 \text{ Hz}$ . Find the power factor and circuit constants and draw its vector diagram. 10

\*\*\*