



C09-EE-306

**3244**

**BOARD DIPLOMA EXAMINATION, (C-09)  
MARCH/APRIL—2016  
DEEE—THIRD SEMESTER EXAMINATION  
ELECTRONICS ENGINEERING**

*Time : 3 hours ]*

*[ Total Marks : 80*

---

**PART—A**

3×10=30

**Instructions :** (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answer should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Define rectifier efficiency and ripple factor.
2. Explain how a Zener diode acts as voltage regulator.
3. Write the applications of photodiode.
4. Briefly explain the working principle of UJT.
5. Write the applications of opto-coupler.
6. Define stability factor.
7. Write the need for multistage amplifier.

/3244

1

[ *Contd...*

[WWW.MANARESULTS.CO.IN](http://WWW.MANARESULTS.CO.IN)

8. Draw a circuit diagram of current series feedback.
9. Classify oscillators based on frequency.
10. Draw the pinout diagram of a 555 timer IC.

**PART—B**

10×5=50

**Instructions :** (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. (a) Explain the working of FW rectifier centre tap transformer using LC filter. 7  
(b) Draw the circuit of HW rectifier with filter. 3
12. (a) Explain the construction and working principle of LED. 7  
(b) Write the applications of LCD. 3
13. (a) Explain DC load line in transistor biasing.  
(b) Explain how transistor works as an amplifier.
14. Draw and explain the operation of a two-stage transformer coupled amplifier.
- \* 15. Explain the working principle of class A power amplifier with diagram.
16. Briefly explain the uses of OP-Amp as an inverter and summing amplifier.
17. Draw and explain the working of a crystal oscillator.
18. Sketch CRT and describe the functions of different parts of CRT.

★ ★ ★