



C09-EE-405

3477

BOARD DIPLOMA EXAMINATION, (C-09)
MARCH/APRIL—2018
DEEE—FOURTH SEMESTER EXAMINATION

DIGITAL ELECTRONICS AND MICROCONTROLLERS

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

- Instructions** : (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. State the De Morgan's theorems.
2. State the need for A/D converters.
3. Classify the different types of memories.
4. Draw the 4-bit shift left register.
5. List the SFRs associated with timer/counter function in 8051.
6. List the features of 8051 microcontroller.
7. Define the terms 'opcode' and 'operand' of an instruction.
8. Explain SWAP A instruction with one example.

/3477

1

[Contd...

WWW.MANARESULTS.CO.IN

9. Define fetch ^{*} cycle and execution cycle.
10. Write an assembly language program to multiply two 8-bit numbers stored in the iRAM locations 40H and 41H. Store the result in 42H and 43H.

PART—B

10×5=50

Instructions : (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. Draw the circuit and explain the working of 4-bit parallel adder using full adders.
12. (a) Convert $A9FC.43_{16}$ into octal number system. 5
(b) Draw the circuit diagram of 2×4 decoder. 5
13. With a neat sketch, explain the working of edge triggered *J-K* flip-flop.
14. Draw the diagram and explain the working of 4-bit asynchronous counter.
15. Draw the pin diagram of 8051 microcontroller and specify the function of each pin.
- * 16. Explain the internal memory organization of 8051 microcontroller.
17. Explain the addressing modes of 8051 microcontroller.
18. Write an 8051 assembly language program along with the comments to find the sum of first 8 natural numbers and save the result at R5 and R6.
