

C09-EE-405

3477

BOARD DIPLOMA EXAMINATION, (C-09) OCT/NOV-2015

DEEE—FOURTH SEMESTER EXAMINATION

DIGITAL ELECTRONICS AND MICROCONTROLLERS

Time: 3 hours [Total Marks: 80

PART—A

 $3 \times 10 = 30$

Instructions: (1) Answer **all** questions.

- (2) Each question carries three marks.
- (3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.
- 1. Convert octal 257·125 into decimal number system.
- **2.** Draw the logic circuit of full-adder using gates and write its truth table.
- **3.** Differentiate between flash ROM and NV RAM.
- **4.** Draw the logic circuit of 4-bit shift right register.
- **5.** Draw the pin diagram of 8051 microcontroller.
- **6.** State the functions of the following:
 - (a) Data pointer
 - (b) Program counter

/**3477** 1 [Contd...

- **7.** Explain SWAP A instruction with one example.
- **8.** Explain any three data transfer group of instructions of 8051 microcontroller.
- **9.** State the addressing mode of each of the following instructions:
 - (a) MOV A, #30 H
 - (b) MOV A, @R0
 - (c) SUBB A, 56 H
 - (d) MOVX A, @DPTR
 - (e) RR A
 - (f) ADD A, R1
- **10.** Write an assembly language program to multiply two 8-bit numbers stored in the iRAM locations 40 H and 41 H. Store the result in 42 H and 43 H.

PART—B

 $10 \times 5 = 50$

Instructions: (1) Answer any **five** questions.

- (2) Each question carries **ten** marks.
- (3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.
- 11. (a) Draw the logic circuit and explain half adder.
 - (b) State and explain De Morgan's theorems.
- **12.** (a) Draw the logic circuit and explain the operation of 4 2 encoder.
 - (b) State the need for A/D and D/A converters.
- **13.** Draw the circuit and explain the operation of master-slave JK flip-flop.

- **14.** Draw the diagram and explain the working of 4-bit asynchronous counter with truth table and waveforms.
- **15.** Describe the memory organization of 8051 microcontrollers.
- **16.** (a) Explain the SBUF register.
 - (b) Draw and explain the bitwise description of PCON register.
- **17.** (a) Distinguish between machine language and assembly language.
 - (b) Classify the 8051 instruction set as per their length with two examples of each.
- **18.** Write an assembly language program along with comments to add two 8-bit numbers stored in the external memory locations 4500H and 4501H. Store the result at 4502H and 4503H.

 $\star\star\star$