

с14-ес-303

4239

BOARD DIPLOMA EXAMINATION, (C-14) OCT/NOV-2017

DECE—THIRD SEMESTER EXAMINATION

ELECTRONIC MEASURING INSTRUMENTS

Time: 3 hours]

/4239

[Total Marks : 80

PART—A 3×10=30

Instructions : (1) Answer **all** questions.

- (2) Each question carries three marks.
- (3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.
- **1.** List the applications of wheatstone bridge.
- 2. Mention the conditions for AC bridge balance.
- **3.** List the factors affecting the accuracy and resolution of a frequency meter.
- 4. List the specifications of digital LCR meter.
- 5. Define the pulse parameters (a) rise time and (b) duty cycle.
- 6. Write the conditions to have flicker-free waveform on CRO.

www.ManaResults.co.in

- 7. Mention any three applications of RF signal generators.
- 8. What is the need for shielding in RF generators?
- 9. Define stray inductance and stray capacitance of a coil.
- 10. What are the needs of plotters and recorders?

PART—B 10×5=50

- **Instructions** : (1) Answer any **five** questions.
 - (2) Each question carries **ten** marks.
 - (3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.
- **11.** Draw the circuit and explain the working of FET input voltmeter.
- **12.** Explain the measurement of capacitance using Schering bridge.
- **13.** Explain the working of successive approximation type digital voltmeter with block diagram.
- 14. (a) List the advantages of digital instruments over analog instruments.5

(b) Explain the working of AF power meter.

5

- **15.** Draw the block diagram and explain the function of each block of general purpose CRO.
- **16.** Explain the procedure for measurement of phase angle and depth of modulation using CRO.
- **17.** Draw and explain the working of function generator with block diagram.
- **18.** Explain the working of *Q*-meter with block diagram.

 $\star\star\star$

AA7(A)-PDF www.ManaResults.co.in

/4239