



C14-EC-403

4457

BOARD DIPLOMA EXAMINATION, (C-14)
OCT/NOV—2016
DECE—FOURTH SEMESTER EXAMINATION
NETWORK ANALYSIS

Time : 3 hours]


[Total Marks : 80

PART—A

3×10=30

- Instructions :** (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

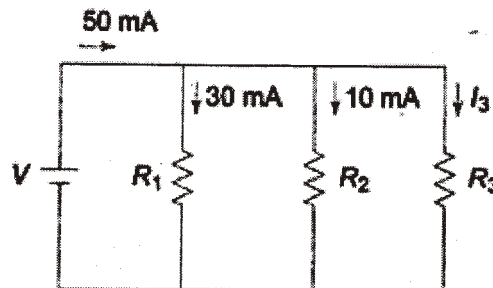1. Define active and passive elements.
2. Determine the current through resistance R_3 .




3. State superposition theorem.
4. State maximum power transfer theorem for DC circuits.

/4457

1

[Contd...

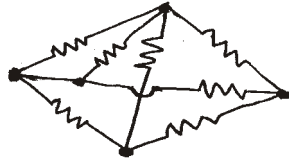5. Determine the number of mesh current equations required for the network shown below.




6. Explain duality of a network.
7. Define steady state and transient response.
8. Define the conditions for symmetry and reciprocity in terms of h -parameters.
9. Draw the circuit of constant resistance equalizer.
10. Define terms Neper and Decibel.

PART—B


10×5=50

- Instructions :** (1) Answer *any five* questions.
 (2) Each question carries **ten** marks.
 (3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

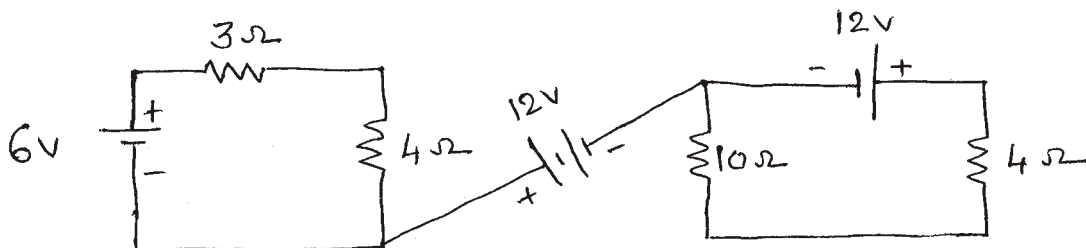
11. (a) Explain the dot rule for coupled circuits. 4
- (b) Find the voltage across A and B in the circuit shown in figure below : 6



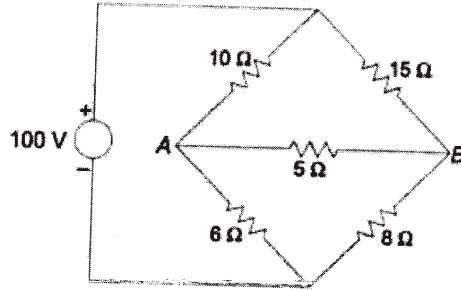
12. Use Thevenin's theorem to find current through 5 ohm resistor in the circuit shown below :



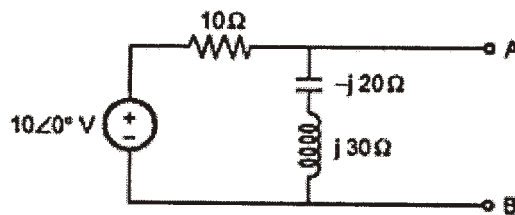
13. Find the load impedance required to be connected across the terminals A-B for the maximum power transfer, in the network shown in the figure below. Also find the maximum power delivered to the load :



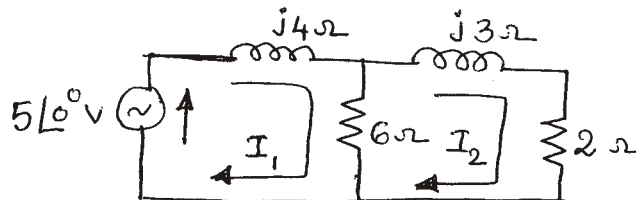
14. Write the mesh current equations for the given circuit and determine the currents I_1 and I_2 :



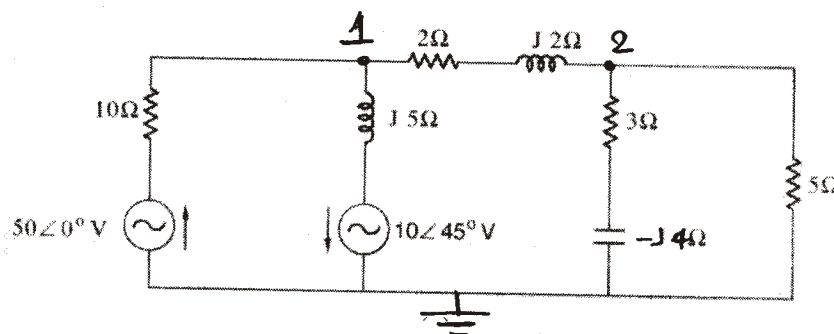15. In the given network find the voltage at node 1 using node voltage method :



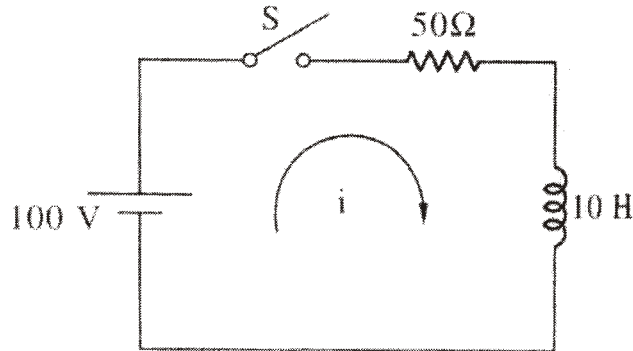16. A series RL circuit with $R = 50 \Omega$ and $L = 10 H$ has a constant voltage $v = 100$ volts applied at $t = 0$ by closing a switch. Find (a) the equations for i , V_R and V_L and (b) the current at $t = 0.5$ second.



17. Derive the expression for characteristic impedance of symmetrical T -network.
18. Determine Y -parameters for the following network :

