

## 4634

## BOARD DIPLOMA EXAMINATION, (C-14) MARCH/APRIL—2017 DECE—FIFTH SEMESTER EXAMINATION

## MICROCONTROLLER APPLICATIONS

[ Total Marks: 80 Time: 3 hours ]

## PART—A

 $3 \times 10 = 30$ 

- **Instructions**: (1) Answer **all** questions.
  - (2) Each question carries **three** marks.
  - (3) Answers should be brief and straight to the point and shall not exceed five simple sentences.
  - 1. What are the factors in selecting an ADC chip?
  - **2.** List the features of MAX1112 ADC chip.
  - 3. Find the number of address lines required for the given memory chips for accessing the data:
    - (a) 8 KB
    - (b) 16 KB
  - **4.** List the types of semiconductor memories.
  - **5.** List the pins of LCD.
  - 6. Draw an interfacing diagram to connect a matrix keyboard.
  - **7.** What is the importance of RTC chip?
  - **8.** List the features of the DS12887 chip.

10.	Draw a block diagram of temperature controller.	
	<b>PART—B</b> 10×5	=50
Inst	<ul> <li>(1) Answer any five questions.</li> <li>(2) Each question carries ten marks.</li> <li>(3) Answers should be comprehensive and the crite for valuation is the content but not the length of answer.</li> </ul>	
11.	Draw and explain the interfacing of temperature sensor LM35 to 8051.	10
12.	Explain data memory space of 8051. Explain, with instructions, how the data is accessed from the data memory.	10
13.	(a) Draw the pin diagram of serial EEPROM chip 24C02 and explain the function of each pin.	6
	(b) Draw the interfacing diagram of 24C02 with 8051.	4
14.	Draw and explain the interfacing of push button switches and LEDs to 8051.	10
15.	Write an assembly language program to communicate with LCD to display "WELCOME". Assume P1 port of 8051 is connected to $D_0$ - $D_7$ of LCD and P2·0 to RS, P2·1 to $R/W$ and P2·2 to $E$ .	
16.	Draw the pin diagram of DS12887 RTC chip and explain the function of each pin.	10
17.	Explain each bit of register-A and register-B of DS12887 RTC chip with neat diagrams.	10
18.	Draw and explain the interfacing of 8051 with a stepper motor.	10

2

AA7(A)—PDF

**9.** What is the need of a solid-state relay?

/4634