

4634

BOARD DIPLOMA EXAMINATION, (C-14)
MARCH/APRIL-2019
DECE - FIFTH SEMESTER EXAMINATION
MICROCONTROLLER APPLICATIONS

Time: 3 Hours]

[Max. Marks: 80

PART - A

3x10=30M

- Instructions:** 1) Answer **all** questions. Each question carries **three** marks.
2) Answers should be brief and straight to the point and shall not exceed five simple sentences.

- 1) Explain the need of signal conditioning in data acquisition system.
- 2) Draw the pin out diagram of ADC0831 and list the features.
- 3) What do you mean by check sum byte of ROM?
- 4) Explain how the semiconductor memories are organized using memory capacity.
- 5) Explain about key debouncing.
- 6) List any six LCD command codes.
- 7) What is the use of RTC?
- 8) Explain the function of PF, PIE bits of DS12887 registers.
- 9) Explain the principle of speed control of DC motor using PWM circuit.
- 10) Explain the need of opto couplers in 8051 microcontroller interface circuits.

*

PART-B

*

5x10=50M

Instructions: 1) Answer any **five** questions.
2) Each question carries **ten** marks.
3) The answer should be comprehensive and the criterion for valuation is the Content but not the length of the answer.

- 11) Draw the interfacing diagram of LM35 with microcontroller through ADC and explain its operation.
- 12) Draw the interfacing diagram of serial EEPROM 24C02 with 8051 microcontroller and explain the operation.
- 13) Draw the memory decoding circuit using 74138 decoder for interfacing of 16KB program ROM with 8051 microcontroller and explain how 8051 access them.
- 14) Draw an interfacing diagram of eight LEDs with p1 port of 8051 microcontroller and write an embedded C program for flashing of LED.
- 15) Explain the interfacing of LCD module with 8051 microcontroller.
- 16) Draw an interfacing diagram of DS12887 RTC with 8051 and explain the sequence of events to sending data to DS12887 and receiving data from DS12887.
- * 17) Draw the pin out diagram of DS 12887 and give the address map of DS12887 RTC.
- 18) Draw an interfacing diagram of stepper motor with port 1 of 8051 microcontroller and write an assembly language program to rotate stepper motor for anticlockwise 360° rotation continuously.

* * *

*