

C14-EC-505

4634

BOARD DIPLOMA EXAMINATION, (C-14) OCT/NOV—2018 DECE—FIFTH SEMESTER EXAMINATION

MICROCONTROLLER APPLICATIONS

Time: 3 hours]

[Total Marks: 80

PART—A

 $3 \times 10 = 30$

Instructions: (1) Answer all questions.

- (2) Each question carries **three** marks.
- (3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.
- **1.** List the features of ADC0809 chip.
- **2.** What is the significance of ADC chip in data acquisition system.
- **3.** Define check sum byte of ROM.
- **4.** List the features of serial EEPROM chip 24c02.
- **5.** What is key-bouncing problem in a keyboard?
- **6.** List any six command codes for programming the LCD.
- 7. List the pins of DS12887 RTC chip.
- **8.** Write the interrupt feature of DS12887 chip.
- **9.** What is the need of opto isolator in interfacing with 8051.
- **10.** How does PWM controls the speed of small DC motor?



[Contd...

WWW.MANARESULTS.CO.IN

PART-B

- *Instructions* : (1) Answer *any* **five** questions.
 - (2) Each questions carries **ten** marks.
 - (3) Answers should be comprehensive and the criteria for valuation are the content but not the length of the answer.
- **11.** Draw and explain the interfacing of DAC0800 to 8051.
- **12.** Draw and explain memory address decoding mechanism using 74LS138 decoder.
- **13.** Draw and explain the interfacing of external 16k x 8 program ROM to 8051.
- **14.** Draw and explain the interfacing of LCD to 8051.
- **15.** Write an assembly language program to identify which key is pressed of 4×4 matrix key board.
- **16.** Draw and explain address map of the DS12887.
- Write an assembly language program for setting time in DS12887 RTC chip.
- **18.** Draw and explain the interfacing circuit for control of a small DC motor using darlington transistor.

* * *

/4634

WWW.MANARESULTS.CO.IN