



C14-EC-606

4740

BOARD DIPLOMA EXAMINATION, (C-14)

MARCH/APRIL—2017

DECE—SIXTH SEMESTER EXAMINATION

DIGITAL CIRCUIT DESIGN THROUGH VERILOG HDL

Time : 3 hours]

[*Total Marks* : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Draw the symbol of CMOS inverter.
2. Draw the stick diagram for NMOS and PMOS transistors.
3. Write a short note on timing simulation.
4. Define module in verilog HDL.
5. Define operand and keyword.
6. Write a short note on arithmetic operators.
7. Write rules for user-define primitives.
8. List the delays used in gate level design.
9. Design JK flip-flop using verilog HDL.
10. Write the applications of PLA.

/4740

1

[*Contd...*

WWW.MANARESULTS.CO.IN

*

PART—B

10×5=50

- Instructions :** (1) Answer *any five* questions.
(2) Each question carries **ten** marks.
(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

- 11.** Explain *n*-well process of CMOS fabrication with diagrams.
- 12.** (a) Compare between verilog HDL and VHDL. 5
(b) Explain the steps involved in design flow for the VLSI IC design. 5
- 13.** Explain all types of operators used in verilog HDL.
- 14.** Explain hierarchical modeling.
- 15.** Design half-subtractor using behavioral, dataflow and structural modeling.
- 16.** Design and write a program for 3 to 3 decoder using verilog HDL.
- 17.** (a) Design and write a program for PIPO shift register. 5
(b) Design and write a program for *D* flip-flop. 5
- 18.** Design and write a program for mealy state machine using verilog HDL.

*
