



C14-EE-402

4462

BOARD DIPLOMA EXAMINATION, (C-14)

MARCH/APRIL—2016

DEEE—FOURTH SEMESTER EXAMINATION

AC MACHINES—I

Time : 3 hours ]

[ Total Marks : 80

**PART—A**

3×10=30

**Instructions** : (1) Answer **all** questions.  
(2) Each question carries **three** marks.  
(3) Answer should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Classify the transformers basing on number of phases and construction.
2. A 100/200 V transformer takes 0.3 A at p.f. of 0.2 lag on open circuit. Find the magnetizing and iron loss component of the no-load current.
3. Explain why the transformer should not be connected to a DC supply.
4. Distinguish between core-type and shell-type transformers.
5. What is the necessity of tap changing in transformer?
6. Write any three advantages of autotransformer.
7. Draw the phasor diagram of an alternator for a lagging power factor load.

8. What are the factors that cause a change of alternator terminal voltage as it is loaded?
9. Define (a) pitch factor and (b) breadth factor.
10. State the conditions for synchronization of an alternator.

**PART—B**

10×5=50

**Instructions :** (1) Answer *any five* questions.  
 (2) Each question carries **ten** marks.  
 (3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. A 33 kV/240 V single-phase transformer is supplied at 240 V on no-load and on low-voltage side. It takes no-load current of 2 A and the power of 60 W. The resistance of the low-voltage winding is 0.8 Ω. Find—

- (a) the power factor on no-load;  
 (b) active current;  
 (c) magnetizing current;  
 (d) copper loss in the LV winding;  
 (e) core loss.

12. A 5 kVA, 220/110 V transformer has the efficiency of 96.97% at 0.8 power factor lagging. Its core loss is 50 W and full-load regulation at 0.8 power factor lag is 5%. Find the efficiency and regulation at  $\frac{3}{4}$  full-load and 0.9 power factor lagging.

13. Draw the equivalent circuit diagram for a 4 kVA, 200/400 V and 50 Hz single-phase transformer from the test results as follows :

OC test : 200 V, 0.8 A, 80 W on LV side

SC test : 20 V, 10 A, 100 W on HV side

Also find the secondary terminal voltage when delivering 10 A at 0.8 power factor lag.

14. (a) State the necessity of parallel operation of single-phase transformers. 5
- (b) Develop the equivalent circuit of a single-phase transformer. 5
15. State the locations and functions of the following with neat sketches :
- (a) Breather
- (b) Explosion vent
- (c) Conservator
- (d) Oil level indicator
16. (a) Explain the working principle of an alternator. 5
- (b) For a 3-phase winding with 4-slot per pole per phase and with the coil span of 10 slots, evaluate the distribution factor and pitch factor. 5
17. A 500 V, 50 kVA, 1-phase alternator has an effective resistance of  $0.2 \Omega$ . A field current of 10 A produces an armature current of 200 A on short circuit and e.m.f. of 450 V on open circuit. Calculate—
- (a) the synchronous impedance and reactance;
- (b) full-load regulation at 0.8 power factor lagging.
18. Two single-phase alternators operating in parallel have induced e.m.fs. on open circuit of  $230 \angle 0^\circ$  and  $230 \angle 10^\circ$ , and having reactances of  $j2 \Omega$  and  $j3 \Omega$  respectively. Calculate—
- (a) terminal voltage;
- (b) power delivered by each of the alternators to a resistive load of  $6 \Omega$ .
- Neglect alternator resistances.

\*\*\*