

с16-ес-401

6435

BOARD DIPLOMA EXAMINATION, (C-16) SEPTEMBER/OCTOBER - 2020 DECE—FOURTH SEMESTER EXAMINATION

LINEAR ICs AND APPLICATIONS

Time : 3 hours]

[Total Marks : 80

PART-A

3×10=30

Instructions : (1) Answer **all** questions.

- (2) Each question carries **three** marks.
- (3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.
- 1. Distinguish between linear and digital ICs.
- 2. Define input impedance and slew rate of an op-amp.
- **3.** Explain the concept of virtual ground.
- 4. Define sweep voltage.
- **5.** Draw differentiator circuit using op-amp.
- 6. Draw the block diagram of PLL.
- 7. Draw the circuit diagram of FM demodulator using PLL.
- 8. List any three applications of current to voltage converter circuit.
- 9. List the advantages of instrumentation amplifier.
- **10.** Define monotonicity and settling time of D/A converter.

/6435

[Contd...

www.manaresults.co.in

PART—B

*

Instructions : (1) Answer any five questions.		
	(2) Each question carries ten marks.(3) Answers should be comprehensive and the crite:	rion
	for valuation is the content but not the length the answer.	
11.	(a) Distinguish between various levels of integration (SSI, MSI, LSI, VLSI, ULSI).	6
	(b) List different types of IC packages and also mention the power rating of each type.	4
12.	(a) Explain the working of differential amplifier constructed using BJTs with diagram.	5
	<i>(b)</i> Explain the operation of fixed negative voltage IC regulator.	5
13.	Explain the working of Wien bridge oscillator using op-amp with neat diagram.	10
14.	Explain the working of monostable multivibrator using op-amp with waveforms.	10
15.	Draw and explain the working of 555 IC based astable multivibrator.	10
16.	(a) Explain the working of VCO (LM 566).	6
	(b) Explain the frequency multiplier using PLL.	4
17.	(a) Explain the working of voltage to current converter circuit.	5
	(b) Explain the pinout diagram of MAX1112 serial ADC.	5
18.	Explain D/A conversion using R-2R ladder network with neat diagram.	10

* * *

2

/6435

*