

**6444**  
**BOARD DIPLOMA EXAMINATION**  
**MARCH/APRIL - 2019**  
**DIPLOMA IN ELECTRICAL AND ELECTRONICS ENGINEERING**  
**ELECTRONICS ENGINEERING - II**  
**FOURTH SEMESTER EXAMINATION**

**Time: 3 Hours****Total Marks: 80**

**PART - A (3m x 10 = 30m)**

*Note 1: Answer all questions and each question carries 3 marks*

*2: Answers should be brief and straight to the point and shall not exceed 5 simple sentences*

1. State the conditions required for sustained oscillations.
2. Draw the circuit diagram of Hartley oscillators
3. List the specifications of 741 IC
4. List design rules for implementing ON-Timer using 555 IC
5. Define Band width of AM wave
6. Define demodulation
7. Draw R-2R ladder network of D/A converter
8. State the need for D/A converter
9. List the advantages and disadvantages of LVDT.
10. State the need of Transducers in Measurement systems

**PART - B (10m x 5 = 50m)**

*Note 1: Answer any five questions and each carries 10 marks*

*2: The answers should be comprehensive and the criteria for valuation is the content but not the length of the answer*

- \* 11. (a) Draw the circuit diagrams of RC phase shift and colpitts oscillators. 6M  
 (b) State the need for Square wave Oscillator 4M
12. (a) Explain the need for AF Oscillator 3M  
 (b) Explain UJT relaxation Oscillator 7M
13. Draw the Pin diagram of 555 IC and explain the function of each pin.
14. (a). Explain the Operational Amplifier as differentiator 7M  
 (b). List the applications of OP Amps 3M
15. (a) Explain the generation of side bands in AM 6M  
 (b) Compare AM and FM 4M

16. Explain D/A conversion using R-2R ladder network
17. (a). Write about Semiconductor Sensors 6M  
(b). List the applications of Sensors 4M
18. (a). Explain the factors influencing the choice of Transducers 6M  
(b). List the applications of Transducers 4M

- xxx -

\*

\*