

7243

**BOARD DIPLOMA EXAMINATION, (C-20)**  
**NOVEMBER/DECEMBER—2022**  
**DECE – THIRD SEMESTER EXAMINATION**  
**NETWORK ANALYSIS**

Time : 3 hours ]


[ Total Marks : 80

**PART—A**


3×10=30

- Instructions :** (1) Answer **all** questions.  
 (2) Each question carries **three** marks.  
 (3) Answers should be brief and straight to the point and shall not exceed five simple sentences.

1. Draw the dual of the given network :

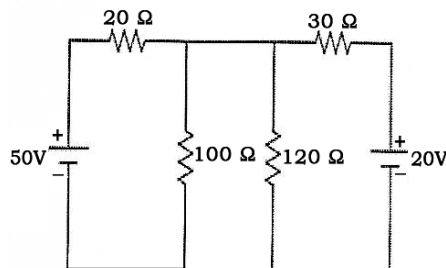

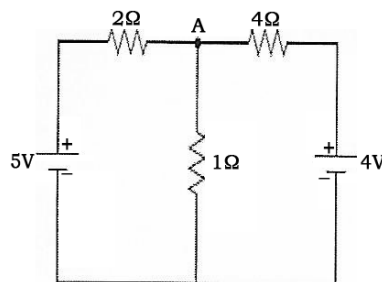2. State reciprocity theorem.  
 3. Define the terms Branch, Junction and Mesh in circuits.  
 4. Find the current  $I$  in the circuit shown below :



/7243

1

[ Contd...


5. Give formula\* for lower cut-off and upper cut-off frequencies.
6. A *RLC* series circuit excited by a 10 v sinusoidal source resonate at a frequency of 50 Hz. If the bandwidth is 5 Hz, what will be the voltage across capacitor?
7. Write Laplace transforms of (a) unit step function, (b) exponential function and (c) sine function.
8. Find the Laplace transform of  $(t + 2)^2 e^t$ .
9. Find the final value of the given function whose Laplace transform is  $I(S) = \frac{S+6}{S(S+3)}$ .
10. Define low pass filter and high pass filter.

**PART—B**

8×5=40

- Instructions :**
- (1) Answer **all** questions.
  - (2) Each question carries **eight** marks.
  - (3) Answers should be comprehensive and criterion for valuation is the content but not the length of the answer.

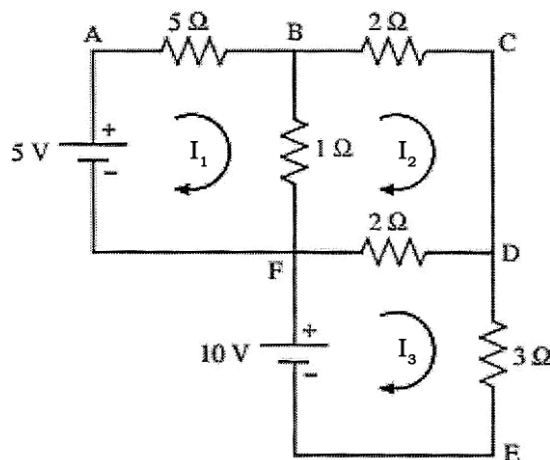11. (a) Solve for mesh currents using Cramer's rule for the given network below :




/7243

2


[ Contd...

\* ( OR )

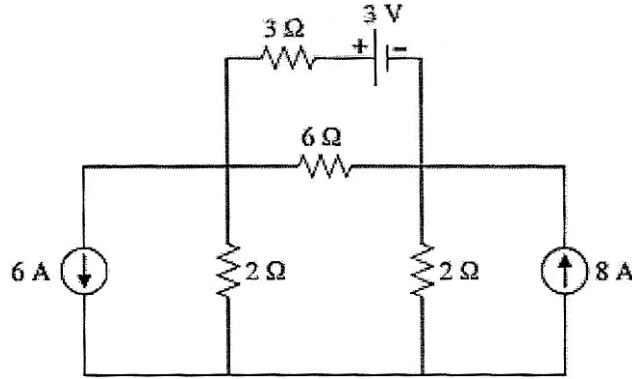(b) Compute the voltage across  $6\ \Omega$  for the circuit shown below :




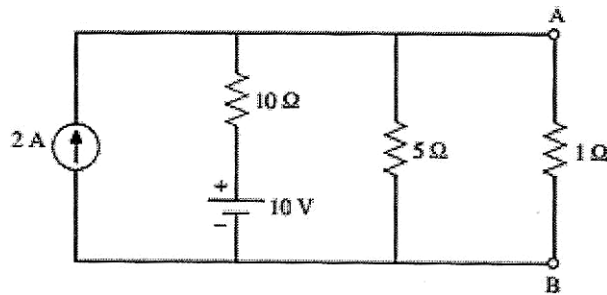12. (a) Find the power loss in the  $1\ \Omega$  resistor of the circuit shown below using Thevenin's theorem.



\* ( OR )

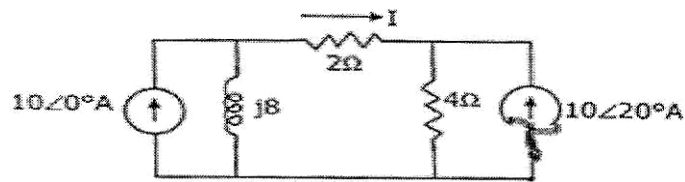(b) Find the current through  $2\ \Omega$  resistor by using superposition theorem.



13. (a) A circuit, having a resistance of  $4.0 \Omega$  with an inductance of  $0.5 \text{ H}$  and a variable capacitance in series, is connected across a  $100 \text{ V}$ ,  $50 \text{ Hz}$  supply. Calculate (i) the capacitance required to attain resonance; (ii) voltages across the inductance and the capacitance at resonance; (iii) the  $Q$  factor of the circuit.

( OR )

- (b) A coil, of resistance  $R$  and inductance  $L$ , is connected in series with a capacitor  $C$  across a variable-frequency source. The voltage is maintained constant at  $300 \text{ mV}$  and the frequency is varied until a maximum current of  $5 \text{ mA}$  flows through the circuit at  $6 \text{ kHz}$ . If, under these conditions, the  $Q$  factor of the circuit is  $105$ , calculate : (a) the voltage across the capacitor; (b) the values of  $R$ ,  $L$  and  $C$ .

14. (a) Explain dc response of an  $RL$  circuit.

( OR )

- (b) Explain second shifting property with one example.

15. (a) Explain  $\pi$  type attenuators with circuit diagram.

( OR )

- (b) Design a constant  $k$  low pass filter to match a line having characteristic impedance of  $500 \Omega$  and to pass frequency up to  $5 \text{ kHz}$ .


\*

**PART—C**

10×1=10

- Instructions :** (1) Answer the following question.  
 (2) The question carries **ten** marks.  
 (3) Answer should be comprehensive and criterion for valuation is the content but not the length of the answer.

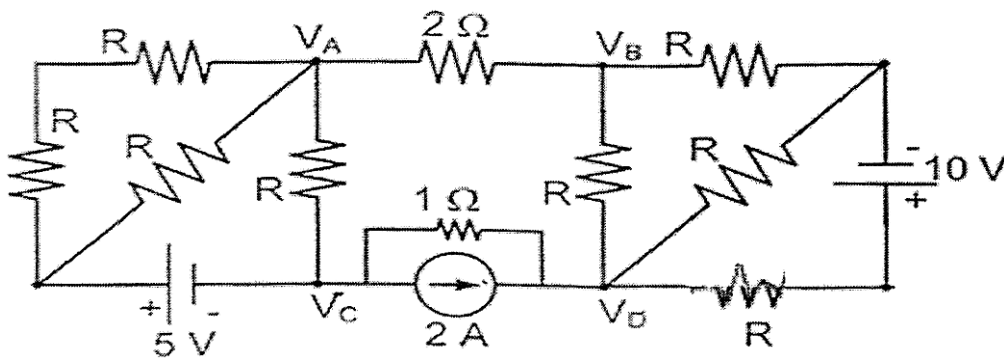16. If  $V_A - V_B = 6 \text{ V}$  then  $V_C - V_D$  is :



\*\*\*

\*

\*