7647

BOARD DIPLOMA EXAMINATION, (C-20)

DECEMBER—2022

DEEE - FIFTH SEMESTER EXAMINATION

POWER SYSTEMS—III (SWITCH GEAR AND PROTECTION)

Time: 3 hours [Total Marks: 80

PART—A

 $3 \times 10 = 30$

Instructions: (1) Answer **all** questions.

- (2) Each question carries **three** marks.
- (3) Answers should be brief and straight to the point and shall not exceed five simple sentences.
- **1.** What is an isolator and state it's application?
- **2.** Classify the different types of circuit breakers.
- **3.** Draw a neat diagram which shows relay coil and circuit breaker connection.
- **4.** Mention any six protective schemes employed for generator.
- **5.** What are the different types of faults in transformers?
- **6.** What are the protective systems for transformers?
- **7.** Write the requirements of bus bar protection.
- **8.** What is the main drawback of differential protection of bus bar?
- **9.** What are the advantages of micro-grid?
- **10.** What is the need of FACTS?

1 [Contd...

PART—B 8×5=40

Instructions: (1) Answer **all** questions.

- (2) Each question carries eight marks.
- (3) Answers should be comprehensive and criterion for valuation is the content but not the length of the answer.
- **11.** (a) Explain the construction and working of MOCB with a neat diagram.

(OR)

- (b) Briefly explain the different types of reactors based on location of reactors.
- **12.** (a) Explain the construction and working of induction type over current relay (non-directional).

(OR)

- (b) Explain the working of definite-distance relay with a neat diagram.
- **13.** (a) Explain the construction and working of a Buchholz relay with a neat diagram.

(OR)

- (b) What are the problems arising in differential protection and precautions (remedies) to be taken for applying differential protection to transformers?
- **14.** (a) Explain the protection of ring main feeder using directional relays.

(OR)

- (b) What is the necessity of bus bar protection? Explain frame leakage protection of bus bar.
- **15.** (a) Explain the translay scheme of protecting transmission line with a neat diagram.

(OR)

(b) Explain circulating-current differential protection to transmission lines. What are the problems in it?

PART—C $10 \times 1 = 10$

- **Instructions:** (1) Answer the following question.
 - (2) The question carries **ten** marks.
 - (3) Answer should be comprehensive and the criterion for valuation is the content but not the length of the answer.
- **16.** Explain the percentage differential protection of a stator of an alternator with a neat diagram.

