

Code No: 113BS**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B.Tech II Year I Semester Examinations, March - 2017****DIGITAL LOGIC DESIGN****(Computer Science and Engineering)****Time: 3 Hours****Max. Marks: 75**

Note: This question paper contains two parts A and B.
 Part A is compulsory which carries 25 marks. Answer all questions in Part A.
 Part B consists of 5 Units. Answer any one full question from each unit.
 Each question carries 10 marks and may have a, b, c as sub questions.

PART- A**(25 Marks)**

- 1.a) Solve for X in the equation $(19.125)_{10} = (X)_8$. [2]
- b) Demonstrate by means of truth table the validity of the DeMorgan laws. [3]
- c) Implement Ex-OR with NOR gates. [2]
- d) Find the min terms of $wxy + yz + x'y$. [3]
- e) Design a 4×1 multiplexer. [2]
- f) How a decoder can be used like DeMux? [3]
- g) What are direct inputs in a flip-flop and why they are used? [2]
- h) What is race around condition? How it is eliminated? [3]
- i) What are the different type of ROMs? [2]
- j) Draw the PLA block diagram. [3]

PART-B**(50 Marks)**

- 2.a) Find 9's complement of 9254.
 - b) Convert $F(A,B,C,D) = \Pi(0,1,2,3,4,6,12)$ to the other canonical form.
 - c) Encode the information character 01101110101 according to the 15 bit Hamming code. [2+4+4]
- OR**
- 3.a) Represent $(524)_{10}$ in 2421 code and BCD Excess-3 code.
 - b) Simplify $x + xyz + yzx' + wx + w'x + x,y$ using Boolean algebra.
 - c) Draw the logic diagram of $(A+B)(C+D)(A'+B+D)$ without simplifying [2+4+4]
- 4.a) Find F' in POS form for $F(A, B, C, D) = \Pi(1, 3, 7, 11, 15) + d(0, 2, 5)$.
 - b) Simplify the function $F(A,B,C,D) = \sum(0,1,3,4,6,8,15)$ using K-Map. [5+5]
- OR**
5. Simplify the function $A'B'CE' + A'B'C'D' + B'D'E' + B'CD' + CDE' + BDE'$ using K-Map and implement using two level AND-OR gates. [10]
 6. Design a BCD to Seven segment display circuit using decoder. [10]
- OR**
- 7.a) Construct a 4-bit Ripple Adder and explain.
 - b) Design a 2-bit magnitude comparator. [5+5]

- 8.a) What is a Master-Slave flip-flop? Explain with block diagram and logic diagram.
b) Design a divide by 6 Ripple Counter using JK flip-flops. [5+5]

OR

- 9.a) What is the difference between edge triggering and level triggering? Explain about Edge triggered D flip-flop with a neat diagram.
b) Design a BCD counter with JK flip-flops. [5+5]
10.a) Given a 32×8 ROM chip with enable input, construct a 128×8 ROM with four chips and decoder.
b) Obtain the PLA program table to realize $F_1(x, y, z) = \sum(2, 4, 6, 7)$ and $F_2(x, y, z) = \sum(0, 3, 4, 5)$. [5+5]

OR

11. Implement the following Boolean functions using PLA: [10]
 $F_1(A, B, C) = \sum(1, 2, 4, 6)$ $F_2(A, B, C) = \sum(0, 1, 6, 7)$
 $F_3(A, B, C) = \sum(2, 6)$ $F_4(A, B, C) = \sum(1, 2, 3, 5, 7)$

---ooOoo---