

Code No: 114DH

**R13**

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**

**B.Tech II Year II Semester Examinations, November/December - 2015**

**PRINCIPLES OF ELECTRICAL ENGINEERING**

**(Electronics and Communication Engineering)**

**Time: 3 Hours**

**Max. Marks: 75**

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.


Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

**PART- A**

**(25 Marks)**

1. a) Explain the time constant of R-L circuit. [2M]
- b) Explain the transient response of source free series RC circuit. [3M]
- c) Define image impedance with a simple 2 port network. [2M]
- d) Find the Z-parameter for the given figure 1. [3M]

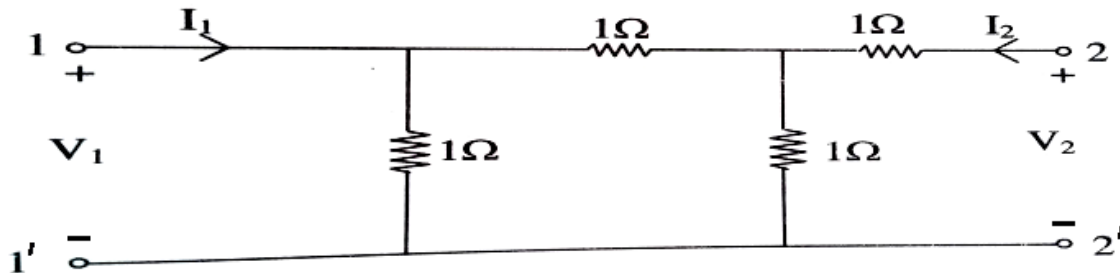


**Figure: 1**

- e) Write about m-derived T-Section filter. [2M]
- f) Explain briefly about Band-Pass and Band-Elimination filters. [3M]
- g) What are the different types of DC Generators? [2M]
- h) Explain the characteristics of DC motors. [3M]
- i) Write the applications of stepper motor. [2M]
- j) A 100 KVA, 1100/230 V, 50Hz, 1- $\phi$  transformer has an HV winding resistance of  $0.1\Omega$  and a leakage reactance of  $0.4\Omega$ . The LV winding has a resistance of  $0.006\Omega$  and a leakage reactance of  $0.01\Omega$ . Find the equivalent winding resistance and reactance referred to HV winding side. [3M]

**PART-B**

**(50 Marks)**

2. Derive the transient response current of RLC circuit for DC excitation. [10]
- OR**
3. Find complete expression for  $i$ , initially no charge on capacitor as shown in figure 2. [10]

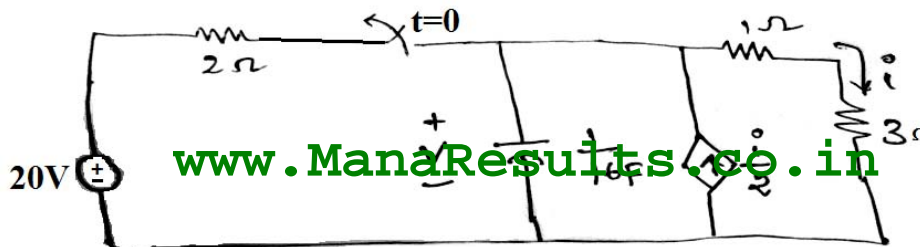

**Figure: 2**

4. For the given circuit find Y-parameters and Transmission-parameters of the circuit shown below figure 3. [10]

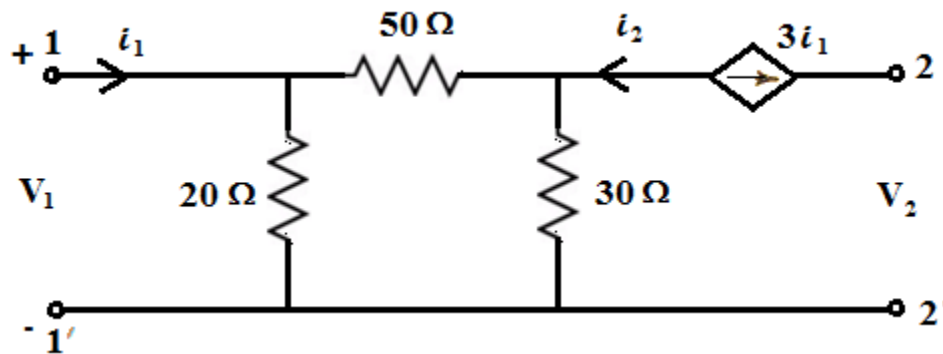


Figure: 3

OR

5. Explain the interconnection of two port network in series and parallel configurations? [10]
6. Derive the characteristic impedance in pass and stop band filters. [10]
- OR
7. Explain the different types of symmetrical attenuators briefly. [10]
8. Explain the principle operation of the DC generator and derive its EMF equation. [10]
- OR
- 9.a) Explain the different speed control methods of DC machine.  
b) Explain the different losses present in DC motor. [5+5]
10. Draw and explain the phasor diagrams of 1- $\phi$  transformer on no-load and load conditions and explain in brief. [10]
- OR
11. Explain the losses present in the transformer and derive the equation of the voltage regulation in 1- $\phi$  transformer. [10]

---ooOoo---