

Code No: 115AF**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B.Tech III Year I Semester Examinations, February/March - 2016****POWER ELECTRONICS****(Electrical and Electronics Engineering)****Time: 3 hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

Part- A**(25 Marks)**

- 1.a) What losses occur in a thyristors during working conditions. [2]
- b) What is the difference between power diode and signal diode? [3]
- c) What is commutation angle or overlap angle. [2]
- d) What is meant by input power factor in controlled rectifier? [3]
- e) What is meant by Duty cycle? [2]
- f) Write down the expressions for average output voltage for step down chopper and step up chopper. [3]
- g) What are the two types of cyclo-converters? [2]
- h) What is meant by step-up and step-down cyclo converters and what are the applications of cyclo converter. [3]
- i) Write the application of inverter. [2]
- j) Draw the circuit diagram of parallel inverter. [3]

Part-B**(50 Marks)**

2. Explain the construction of SCR with neat diagram. Draw its V-I characteristics. [10]
- OR**
3. Explain the operation of IGBT with VI and switching characteristics. [10]
 4. A single phase semi converter delivers to RLE load with $R=5\Omega$, $L=10\text{mH}$ and $E=80\text{V}$. The source voltage is 230V, 50Hz. For continuous conduction, Find the average value of output current for firing angle $\alpha=50^\circ$. [10]

OR

5. Discuss the operation of single phase semi converter and derive the output voltage expression. [10]
6. What is chopper and how they are classified. Explain the working of A.C chopper. [10]

OR

7. A dc chopper is supplying a resistive load. If the input and output voltages are 200V and 120V and the chopping frequency is 800Hz, find the periods of conduction and blocking in each cycle. [10]
8. What is an Ac voltage controller? List some of its industrial applications. Enumerate its merits and demerits. [10]

OR

9. A single-phase voltage controller has input voltage of 230 V, 50 Hz and a load of $R=15\ \Omega$. For 6 cycles on and 4 cycles off, determine
a) r.m.s output voltage, b) input pf c) average and r.m.s thyristor currents. [3+3+4]
10. Explain the operation of single pulse modulation of inverter with neat diagram. [10]
- OR**
11. Draw and explain the operation of three-phase series-inverter circuit. [10]

--ooOoo--