

Code No: 115AF

## JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year I Semester Examinations, November - 2015

## POWER ELECTRONICS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 75

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A. Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

**PART - A (25 Marks)**

- 1.a) What are the applications of power MOSFET? [2]
- b) What are the factors that affect the turn off time of SCRs? [3]
- c) What is phase control technique? [2]
- d) What are the applications of dual converters? [3]
- e) What is an AC chopper? [2]
- f) What are the different kinds of power losses in Choppers? [3]
- g) What is an AC voltage controller? [2]
- h) What are the applications of Cyclo converters? [3]
- i) What is sinusoidal PWM technique? [2]
- j) What are the applications of parallel inverter? [3]

**PART - B (50 Marks)**

- 2.a) Explain in detail about the series connection of SCRs.
- b) Following are the specifications of a Thyristor operating from a peak supply of 400V:  
 Repetitive peak current  $I_p = 200A$ ,  $\left(\frac{di}{dt}\right)_{max} = 50 \frac{A}{\mu s}$ ,  $\left(\frac{dv_a}{dt}\right)_{max} = 180 \frac{V}{\mu s}$ .  
 Design a Snubber circuit if the minimum load resistance is  $15\Omega$ . Take damping ratio as 0.7 and the factor of safety as 2 [5+5]

**OR**

- 3.a) What are the main specifications and ratings of SCR to be considered while designing? Explain.
- b) An UJT circuit has the following parameters:  
 $\eta = 0.67$ ,  $V_D = 0.6V$ ,  $I_v = mA$ ,  $V_v = 1V$ ,  $I_p = 10 \mu A$ ,  $V_{BB} = 20V$   
 Find the values of  $V_{FE}$  so as to turn on UJT if  $R_E$  is (i)  $1 k\Omega$  (ii)  $1500 \Omega$  [5+5]
- 4.a) Derive the expression for the average load voltage of single phase half controlled converter with RLE load.
- b) A three phase half wave SCR converter delivers constant load current of 20A over the firing angle range of  $0^\circ$  to  $60^\circ$ . At these two firing angles, compute the power delivered to load for an ac input voltage of 300V from a delta star transformer. [5+5]

**OR**

- 5.a) Derive the expression for the RMS load voltage of six pulse converter with R load.
- b) In a single phase midpoint converter turns ratio from primary to each secondary is 2. The source voltage is 230V, 50 Hz. For a resistive load of  $5\Omega$ , calculate the maximum value of average output voltage and load current and the corresponding firing and conduction angles [5+5]

- 6.a) Explain in detail about the time ratio control.  
b) A step down chopper is fed from 200V DC and its duty cycle is 0.6. Calculate the RMS value of output voltages for fundamental and third harmonic components. [5+5]

**OR**

- 7.a) Derive the expression for the output voltage of step up chopper.  
b) A chopper fed from a 200V DC source, is working at a frequency of 50 Hz and is connected to an RL load of  $R = 4\Omega$  and  $L = 30$  mH. Determine the value of duty cycle at which the minimum load current will be (i) 5 A (ii) 10 A [5+5]

- 8.a) Explain the operation of a single phase mid-point step up cyclo converter with the help of circuit diagram and waveforms  
b) A single phase voltage controller with resistive load has the following data: supply mains: 230V, 50 Hz,  $R = 5\Omega$ . Calculate the firing angle at which the greatest forward or reverse voltage is applied to either of the thyristors and the magnitude of these voltages [5+5]

**OR**

- 9.a) Explain the operation of a single phase bridge type step down cyclo converter with the help of circuit diagram and waveforms  
b) A single phase voltage controller with RL load has the following data: Supply mains: 230V, 50 Hz,  $Z = (3+j4)\Omega$ . Calculate the control range of firing angles and the maximum value of RMS load current [5+5]

- 10.a) Draw the circuit diagram of a single phase half bridge inverter and explain its operation.  
b) A three phase bridge inverter delivers power to a resistive load from a 400V DC source. For a star connected load of  $8\Omega$  per phase, determine RMS value of load current and RMS value of thyristor current for  $120^\circ$  conduction mode of operation. [5+5]

**OR**

- 11.a) Explain the  $180^\circ$  conduction mode of operation of three phase inverters with necessary circuit diagram and waveforms.  
b) A single phase bridge inverter is fed from a 200 DC. In the output voltage wave, only fundamental component of voltage is considered. Determine the RMS current ratings of an SCR and a diode of the bridge for a resistive load of  $R = 5\Omega$ . [5+5]

---ooOoo---