

Code No: 115AH**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B. Tech III Year I Semester Examinations, November/December - 2018****IC APPLICATIONS****(Electrical and Electronics Engineering)****Time: 3 hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A. Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART - A**(25 Marks)**

- 1.a) Define Monolithic and Hybrid IC Technologies. [2]
- b) What are the advantages of ICs over discrete circuits? [3]
- c) Define Input and Output Offset-voltages. [2]
- d) Compare Open loop and Closed loop configurations of Op-Amp. [3]
- e) What is the use of VCO? [2]
- f) Compare 1st order Low Pass and High Pass filters. [3]
- g) Draw the block diagram for PLL. [2]
- h) Distinguish between Astable and Monostable Multi-vibrators. [3]
- i) Which is the fastest ADC and why? [2]
- j) For a particular 8-bit ADC, the conversion time is 9 μ s. Find the maximum frequency of an input sine wave that can be digitized. [3]

PART - B**(50 Marks)**

- 2.a) Draw 2-input TTL NAND gate and explain its operation with the help of functional table.
- b) Draw the CMOS transmission gate and realize a 2 \times 1 MUX using this transmission gate. [5+5]

OR

- 3.a) Draw the CMOS circuit diagram of Tri-State Buffer? Explain the circuit with the help of logic diagram and function table.
- b) What is the necessity of separate interfacing circuit to connect CMOS gate to TTL gate? Draw the interface circuit and explain the operation? [5+5]
4. Draw the circuit and explain the operation of Instrumentation Amplifier. Derive the expression for its output voltage. [10]

OR

- 5.a) An Op-Amp has a differential gain of 80 dB and CMRR of 95 dB. If $V_1 = 2 \mu$ V and $V_2 = 1.6 \mu$ V, then calculate differential and common mode output values.
- b) Explain the principle of operation of Sample and Hold circuit. [5+5]

6. Draw the basic circuit of RC - Phase Shift Oscillator and explain its operation. Also derive the expression for frequency of Oscillation. [10]

OR

- 7.a) Design first order high pass filter with a cut off frequency of 10 KHz with a pass band gain of 1.5.
b) Explain various types of filters along with their frequency response. [5+5]
- 8.a) Derive the expression for the Duty cycle of an Astable Multi-vibrator using IC555.
b) Compare and contrast Schmitt trigger and Comparator. [6+4]

OR

- 9.a) Derive an expression for Capture Range of PLL.
b) Show that the Lock-in Range of a PLL is given by $\Delta f_L = \pm 7.8 f_o / V$, Where the symbols used have the usual meaning. [5+5]
- 10.a) Find the Resolution of 12-bit D/A Converter.
b) An 8-bit Successive Approximation ADC is driven by a 1 MHz clock. Find its Conversion time. [5+5]

OR

- 11.a) Obtain an expression for the output voltage of R-2R DAC.
b) Explain how Dual Slope A/D converter provides Noise rejection. [5+5]

---ooOoo---