

**R15****Code No: 124CV****JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B.Tech II Year II Semester Examinations, April - 2018****ELECTRONIC CIRCUIT ANALYSIS****(Common to ECE, EIE, ETM)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

**PART- A****(25 Marks)**

- 1.a) Draw the circuit diagram of Darlington Pair. [2]
- b) What is the expression for harmonic distortion in single stage amplifiers? [3]
- c) Define Gain-Bandwidth Product in detail. [2]
- d) Draw the Small signal model of MOS amplifier. [3]
- e) List out the Conditions for Oscillations in detail. [2]
- f) Explain different Classification of Feedback Amplifiers. [3]
- g) Define Thermal Stability and Thermal Runway. [2]
- h) What is Heat sink and explain its advantages? [3]
- i) Define Q factor. [2]
- j) What is the expression for harmonic distortion in tuned amplifiers? [3]

**PART-B****(50 Marks)**

- 2.a) Discuss about effect of  $C_b$  on frequency response of RC coupled amplifier.
- b) Draw the circuit diagram of Direct Coupled Amplifier and explain its operation in detail. [5+5]

**OR**

- 3.a) With a neat circuit diagram. Explain about Boot-Strap emitter follower amplifier.
  - b) Derive the Analysis of CE amplifier with Emitter Resistance and explain its operation along with circuit diagram. [5+5]
- 4.a) Find the voltage gain, input and output resistances of a emitter follower at high Frequencies.
  - b) A common source amplifier uses a MOSFET with the following parameters  $g_m=1.5\text{mA/V}$ ,  $r_d=40\text{kohms}$ ,  $C_{gs}=3\text{pF}$ ,  $C_{ds}=1\text{pF}$ ,  $C_{gd}=3.2\text{pF}$ . The value of  $R_d=200\text{Kohms}$ . The amplifier operates at 30KHz. Find Voltage gain, input resistance, output resistance and input capacitance. [5+5]

**OR**

- 5.a) Draw the circuit diagram of Common source amplifier with Resistive load and explain its operation.
- b) Derive the expression for  $f_T$  of a transistor in detail. [5+5]

- 6.a) Derive the expression for frequency of oscillation of BJT RC phase-shift oscillator with necessary explanation.
- b) What is the equivalent circuit of a crystal? Derive the expressions for series and parallel resonances. A crystal oscillator has the following parameters:  $L=0.33\text{H}$ ,  $C=0.065\text{pF}$ ,  $C_m=1.0\text{pF}$  and  $R=5.5\text{ k ohm}$ .
- i) Find the series resonant frequency.
- ii) Find the Q of the crystal. [5+5]

**OR**

- 7.a) Draw the block diagrams of four types of negative feedback amplifier circuits and explain the advantages and disadvantages with necessary derivations.
- b) Explain why RC Phase shift oscillators are not used at high frequencies. [5+5]
- 8.a) Explain the operation of a class A push-pull power amplifier and list out its advantages and disadvantages.
- b) A single transistor is operating as an ideal class B amplifier with a 10-K load. A dc meter in the collector circuit reads 8mA. How much signal power is delivered to the load? [5+5]

**OR**

- 9.a) Draw the circuit diagram of Complementary Symmetry Class B Push-Pull Amplifier and explain its operation.
- b) List out the few difference between Class A, Class B and Class AB Push-Pull amplifiers with examples. [5+5]

- 10.a) What is a stagger tuned amplifier? Explain its advantages and disadvantages.
- b) Write short notes on Small Signal Tuned Amplifiers in detail. [5+5]

**OR**

- 11.a) What are the different Effect of Cascading Single Tuned Amplifiers on Bandwidth in detail.
- b) Explain the concept of Stability of Tuned Amplifiers with one example. [5+5]

**---ooOoo---**