

Code No: 125EB

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B. Tech III Year I Semester Examinations, November/December - 2017****LINEAR AND DIGITAL IC APPLICATIONS**

(Common to ECE, ETM)

Time: 3 hours**Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A. Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART - A**(25 Marks)**

- 1.a) Define input offset voltage. [2]
- b) List features of 741 op-amp. [3]
- c) Discuss about all pass filters. [2]
- d) List the application of 565 PLL. [3]
- e) List different ADC and DACs. [2]
- f) List specifications of DAC. [3]
- g) Which of the parameters decide the fan out and how? [2]
- h) Explain noise margin and propagation delay with respect to CMOS logic. [3]
- i) What is race around condition? How is it avoided? [2]
- j) Explain one application of SR latch. [3]

PART - B**(50 Marks)**

2. Draw the circuit diagram of a two input non-inverting type summing amplifier and derive the expression for the output voltage. [10]

OR

3. Explain the working of instrumentation amplifier with suitable diagram. [10]

4. Draw the block diagram of 565 PLL and explain about each block. Make circuit connections to track the input signal and explain its operation. [10]

OR

5. Design a wide band pass filter with $f_L=500$ Hz and $f_H = 2$ KHz, and a pass band again = 5 for both sections of filter. Also determine the value of Q for the filter. [10]

6. Which is the fastest ADC? Explain the operation and discuss its merits and de-merits. [10]

OR

7. With a neat diagram explain the working principle of R-2R ladder type DAC. [10]

8. With neat circuit diagram explain the working of a 4-bit odd parity generator. [10]
OR
9. Design 16×1 multiplexer using 4×1 multiplexer. [10]
10. Design a modulo 12 ripple counter using 74×74 . [10]
OR
11. How many address and data lines are required to access all the locations of dynamic RAM cell arrays specified below? [10]
a) $4M \times 4$ b) $1M \times 1$ c) $1M \times 4$ d) $4M \times 1$

---ooOoo---