

Code No: 126AG

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B. Tech III Year II Semester Examinations, April - 2018****COMPUTER METHODS IN POWER SYSTEMS****(Electrical and Electronics Engineering)****Time: 3 hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A. Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART - A**(25 Marks)**

- 1.a) Define the terms TREE, Co-TREE and LINK of a graph. [2]
- b) What is an incidence Matrix? Explain with a suitable example. [3]
- c) What is necessity of power flow studies? [2]
- d) Compare all load flow methods. [3]
- e) What is the necessity of short circuit analysis? [2]
- f) List out the advantages of per unit representation for power systems. [3]
- g) Define steady state, dynamic and transient stability. [2]
- h) Define synchronizing power coefficient. [3]
- i) Give the limitations of equal area criterion. [2]
- j) What are the methods to improve transient stability? [3]

PART - B**(50 Marks)**

- 2.a) Form the Y_{BUS} for the system shown in below figure 1, using singular transformation method.

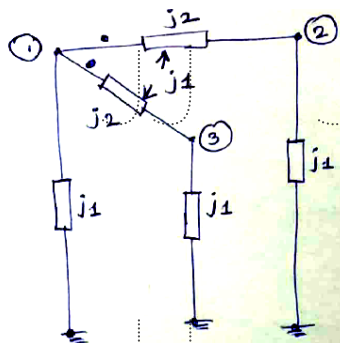


Figure 1

- b) Give the steps for modification of existing Z_{BUS} , when a branch Z_b is added from existing bus(k) to the reference bus. [5+5]

OR

- 3.a) Show that $Y_{BUS} = A^T Y_{pre} A$.
 b) Form the Z_{BUS} for the system shown in below figure 2.

[5+5]

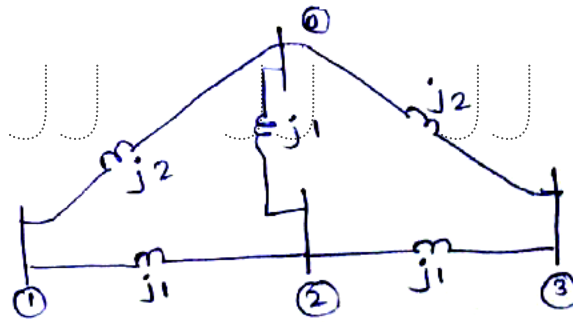


Figure 2

- 4.a) Briefly discuss about the classification of load flow methods and their application in the real world.
 b) For the three bus system shown in below figure 3, perform 2 iterations of Gauss Seidal load flow method. The value shown in figure are line reactances in p.u. and shunt capacitor of susceptance $J0.2$ per unit.

[5+5]

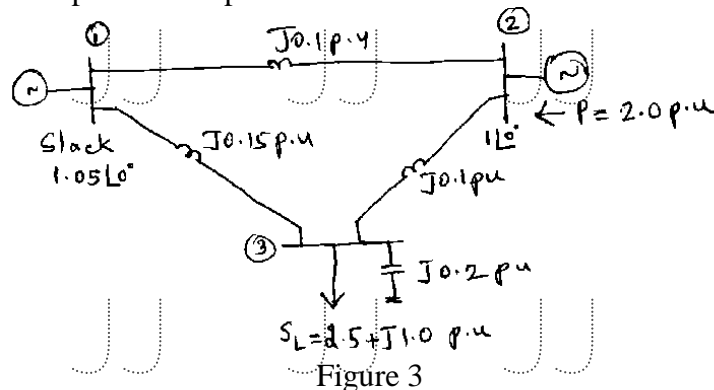


Figure 3

OR

5. Explain the Newton Raphson Load flow method in polar force, and derive the equation to compute the Jacobian matrix elements. [10]
 6. For the system shown in figure 4 below. All values shown are per unit reactance on their own basic.

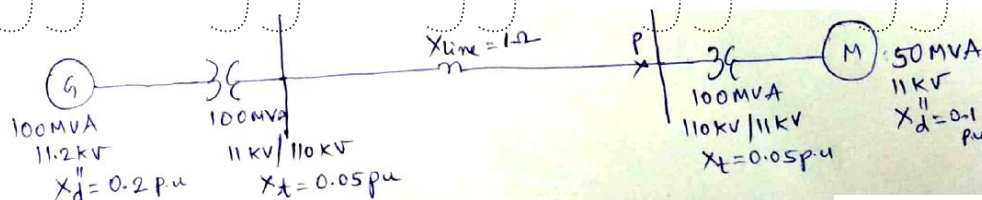


Figure 4

- a) Draw the single line reactances diagrams of the system with system base as 100 MVA and 11.2 kV.
 b) Determine the symmetrical sub transient fault current for a balanced fault at point 'P'.

[5+5]

OR

- 7.a) Determine the sequence currents for the system of un balanced phase currents as given below are drawn by a balanced delta load with $Z_{\text{phase}} = j10 \Omega$.

$$I_a = 10 \angle 0^\circ, I_b = 10 \angle 180^\circ, I_c = 0^\circ$$

- b) For the system shown in figure 5, find the fault current for a LG fault at print 'P'. Assume fault load current to be zero. [5+5]

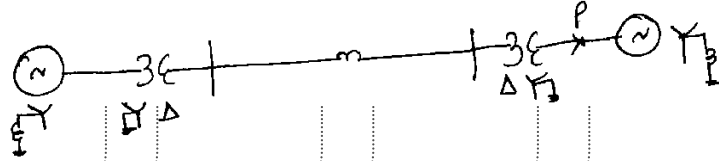


Figure 5

Generator: 100 MVA, 11 kV, $X_1 = X_2 = j0.2 \text{ pu}$, $X_0 = j0.05 \text{ pu}$, $X_n = j0.3 \text{ pu}$.

Transformer1 & 2: 100 MVA, 11 kV/33kV, $X_1 = X_2 = j0.01 \text{ pu}$, $X_0 = j0.012 \text{ pu}$

Transmission Line; 33 kV, 100 MVA, $X_1 = X_2 = j0.02 \text{ pu}$, $X_0 = j0.05 \text{ pu}$

System Motor: 100 MVA, 11 kV, $X_1 = X_2 = j0.15 \text{ pu}$, $X_0 = j0.05 \text{ pu}$ and $X_n = j0.2 \text{ pu}$.

- 8.a) What is steady state stability limit? Derive the necessary condition for the system to be steady state stable.
- b) For an SMVB system shown in below figure 6, the following are the operating conditions: $V_\infty = 1 \angle 0^\circ$, $|V_t| = 1.0$, line reactance $jx = 0.1$ per unit and sub transient reactance of the synchronous machine is $X''_d = j0.2 \text{ pu}$.

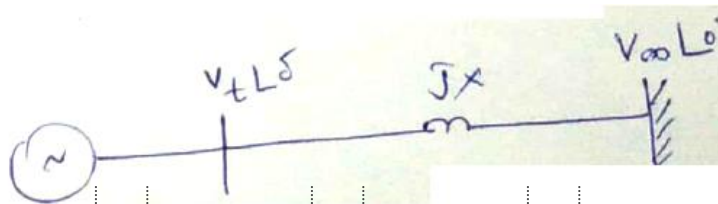


Figure 6

Determine the power angle curve of the machine. Assume $\rho_m = \rho_e = 1.0$.

[5+5]

OR

- 9.a) Briefly discuss about the methods to improve steady state stability.
- b) What is power angle curve? Deduce the relation from a SMIB system having lossless line. [5+5]
- 10.a) What is swing and derive the swing equation?
- b) Give the applications of equal area criterion. [5+5]

OR

11. For the system shown in below figure 7.

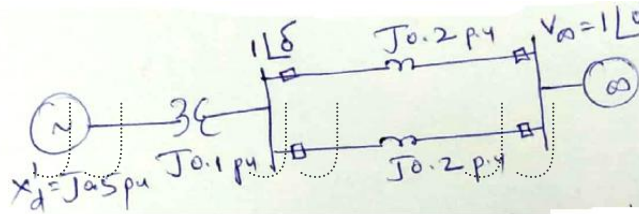


Figure 7

a) Determine the maximum permissible increase in ρ_m (mechanical input power) that is possible to lead the system in to critical stability. Assume initially $\rho_m = \rho_e = 1.0$ pu.

b) Determine the critical clearing angle, when a 3 d balanced fault occurs at the middle of the second line and the fault is cleared by operating the line using CB's at both ends.

[5+5]

---ooOoo---