

Code No: 126AH

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B. Tech III Year II Semester Examinations, December - 2017****ELECTRICAL AND ELECTRONICS INSTRUMENTATION****(Electrical and Electronics Engineering)****Time: 3 hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A. Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART - A**(25 Marks)**

- 1.a) How can you extend the range of an ammeter? [2]
- b) Enlist the advantages of PMMC instrument. [3]
- c) Compare AC and DC potentiometers. [2]
- d) How can you measure unknown resistance using DC potentiometers? [3]
- e) What are the main sources of errors in energy meters? [2]
- f) Draw the circuit diagram of three phase power measurement using 2 wattmeters method. [3]
- g) What are the DC measuring bridges? [2]
- h) Draw the circuit diagram of Owen's bridge and write the application of its. [3]
- i) What are the applications of CRO? [2]
- j) What are the main characteristics the transducers? [3]

PART - B**(50 Marks)**

- 2.a) A basic d' Arsonval meter movement with an internal resistance, $R_m = 100\Omega$ and a full scale current of $I_{wm} = 1mA$ is to be converted in to a multi range D.C. voltmeter with ranges of 0-10V, 0- 50V, 0- 250V and 0-500V. Find the values of various resistances required for potential divider arrangement.
- b) Explain the principle of operation of Quadrant electrometer type Electrostatic voltmeter and mention its applications. [5+5]

OR

- 3.a) Describe the construction and working principle of attraction type moving iron instrument.
- b) How can you extend the range of Electro static Voltmeters? Explain. [5+5]
- 4.a) Explain the Principle of operation of Polar type AC potentiometer with a neat sketch.
- b) What is the need of Potential transformer? And describe about different errors occurred in PTs. [5+5]

OR

- 5.a) Reduce the ratio error of current transfer with necessary sketches.
- b) What are the types of instrument transformers? Compare them. [5+5]

- 6.a) Prove that for electro-dynamometer type wattmeter
true power = $\{\cos \Phi / [\cos \beta \cos (\Phi - \beta)]\}$ x actual wattmeter reading
Where $\cos \Phi$ = power factor of the circuit
 $\beta = \tan^{-1} (\omega L/R)$ where L and R are the inductance and resistance of the pressure coil of the circuit.
- b) Explain the operation of induction type energy meter and explain how you can provide overload compensation to it. [5+5]

OR

- 7.a) How can you test energy meter by phantom loading? Explain with a neat sketch.
- b) Explain the construction and working of three element wattmeter with a neat sketch. [5+5]

- 8.a) Draw the block diagram of wheatstone bridge with digital readout and explain its operation.
- b) Draw the circuit diagram of Maxwells inductance bridge and derive a relation for unknown Inductance. [5+5]

OR

- 9.a) How could you measure insulation resistance using loss of charge method? Describe with the help of diagram.
- b) Draw the circuit diagram of Schering bridge and derive a relation for unknown capacitance. [5+5]

- 10.a) Explain the working of CRT with a neat sketch.
- b) What is the principle of strain gauge? And derive a relation for gauge factor. [5+5]

OR

- 11.a) Explain the working principle of Thermistors, mention advantages and applications of them.
- b) Describe the principles of operation of capacitive transducers and mention their applications. [5+5]

---ooOoo---