

Code No: 132AJ

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD
B.Tech I Year II Semester Examinations, August/September - 2017
BASIC ELECTRICAL AND ELECTRONICS ENGINEERING
(Common to CE, ME, MCT, MMT, MIE, CEE, MSNT)

Time: 3 hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A. Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART- A

(25 Marks)

- | | |
|-------------------------------------------------------|-----|
| 1.a) Define Independent and dependent sources. | [2] |
| b) What is complex power? Explain. | [3] |
| c) What is Q-factor? Explain. | [2] |
| d) State and explain Norton's theorem. | [3] |
| e) Define Forward and Reverse Resistances of a diode. | [2] |
| f) What are the advantages of bridge rectifier? | [3] |
| g) Substantiate the need of biasing a BJT. | [2] |
| h) Explain how a BJT acts as an current amplifier. | [3] |
| i) Compare BJT and JFET. | [2] |
| j) Explain Zener Breakdown mechanism. | [3] |

PART-B

(50 Marks)

- 2.a) Write short notes on Star – Delta transformation.
- b) Find the equivalent resistance across the terminals A-B as shown in Figure 1. [5+5]

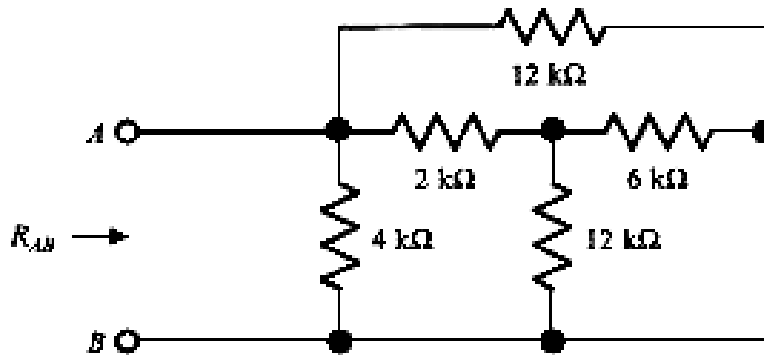


Figure: 1
OR

- 3.a) Illustrate following terms:
 i) Impedance ii) Reactance iii) Phase deference iv) Power factor.
- b) Find the impedance of series R-L-C circuit with $R=100\Omega$, $X_L=50\Omega$ and $X_C=20\Omega$. [6+4]

- 4.a) What is parallel resonance? Explain.
 b) Derive an expression for the resonant frequency for a parallel circuit shown in below Figure 2. [4+6]

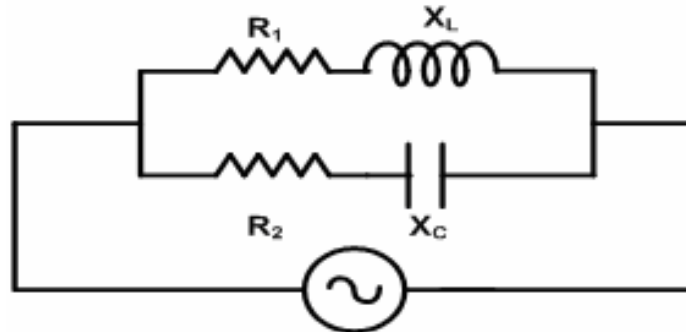


Figure: 2
OR

- 5.a) State and Explain Tellegen's theorem.
 b) Find the value of R_L that will absorb the maximum average power for the circuit shown in Figure 3. Calculate that power. [4+6]

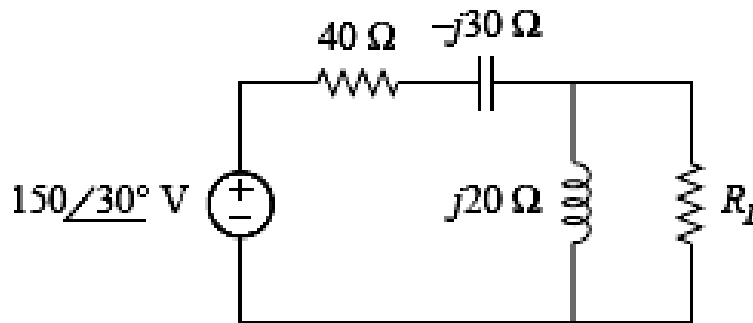


Figure: 3

- 6.a) Draw load line on the V-I characteristics of a PN junction diode and highlight its significance in diode operation.
 b) Differentiate between transition and diffusion capacitances of a diode. [6+4]
 OR
 7.a) Compare the characteristics of L section, capacitor and π -filters.
 b) Derive an expression for the ripple factor of a full-wave rectifier using Induction filter. [3+7]
 8.a) Explain about Fixed Bias Circuit. List its deficiencies.
 b) Derive the expression for the stability "S" of a voltage divider bias Circuit. [5+5]
 OR
 9.a) Determine the h-parameters from the characteristics of BJT in CB configuration.
 b) Compare the performance of a transistor in different configurations. [6+4]
 10.a) Draw JFET small signal model. Establish a relation between μ , g_m and r_d .
 b) Explain the significance of pinch-off voltage on JFET operation. [5+5]
 OR
 11.a) Explain the operation of Tunnel diodes with the help of its V-I characteristic curve.
 b) Justify the statement 'A zener diode can be used as a voltage regulator'. [6+4]