

Code No: 134CF

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B.Tech II Year II Semester Examinations, December - 2019****SWITCHING THEORY AND LOGIC DESIGN****(Common to EEE, ECE, MCT, ETM)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b as sub questions.

**PART – A****(25 Marks)**

- 1.a) What is unit distance code? [2]
- b) What are the basic operations in Boolean algebra? [3]
- c) Why subtractor ICs not available? [2]
- d) What is a priority encoder? [3]
- e) What are the basic types of shift registers? [2]
- f) What are the various methods used for triggering flip-flops? [3]
- g) List the features of sequential circuits. [2]
- h) What is a Modulo-N counter? What are the applications of this counter? [3]
- i) Explain capabilities of finite state machine. [2]
- j) Define Merger graph of n-state machine M. [3]

**PART – B****(50 Marks)**

- 2.a) Covert  $105.15_{10}$  to binary, octal, hexadecimal.
  - b) What is hamming code? How is the hamming code word tested and corrected. [5+5]
- OR**
- 3.a) Simplify the following Boolean expressions using the Boolean theorems.
    - i)  $(A+B+C)(B'+C) + (A+D)(A'+C)$
    - ii)  $(A+B)(A+B')(A'+B)$
  - b) Why a NAND and NOR gates are known as universal gates? Simulate all the gates. [5+5]
- 4.a) Simplify the expression  $Y = \sum m(7,9,10,11,12,13,14,15)$  using the k-map method.
  - b) Simplify the following Boolean function  $F(A,B,C,D) = \sum m(1,3,7,11,15) + \sum d(0,2,5)$ . [5+5]

**OR**

- 5.a) Explain the differences between a MUX and a DEMUX. Realize 16-input multiplexer by cascading of two 8-input multiplexers 74151.
  - b) Realize the function  $f(A,B,C,D) = \prod [(1,4,6,10,14) + d(0,8,11,15)]$  using (i) 16:1 MUX (ii) 8:1 MUX. [5+5]
- 6.a) Realize D-FF and T-FF using JK-FF. Draw the logic diagrams with their truth tables.
  - b) Deduce the design procedure for sequential logic circuits and give the classification of sequential logic circuits. [5+5]

**OR**

- 7.a) Design, draw and explain a synchronous MOD-12 down-counter using j-k flip-flop.
- b) Design, draw and explain a 4-bit ring counter using D- flip flops with relevant timing diagrams. [5+5]

- 8.a) Explain in detail about serial binary adder with neat logic diagram.  
 b) Draw a state diagram for the sequential machine whose output is '1' when the sequence is 01. [6+4]

**OR**

- 9.a) Discuss about the approaches of designing synchronous sequential finite state machines.  
 b) Design a 1101 sequence detector and draw its logic diagram. [5+5]

- 10.a) What are the Moore and Melay machines? Compare them.  
 b) Explain the procedure for state minimization using the partition technique. [4+6]

**OR**

- 11.a) Reduce the following machine shown below.

PS	NS, Z	
	X = 0	X = 1
A	B,0	C,1
B	B,0	A,1
C	A,1	E,0
D	B,1	C,1
E	A,0	D,0

- b) Explain concept of minimal cover table. [4+6]

---ooOoo---