

Code No: 137JD**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B. Tech IV Year I Semester Examinations, December - 2019****VLSI DESIGN****(Common to ECE, EIE)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A. Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b as sub questions.

PART – A**(25 Marks)**

- 1.a) Write the equation for threshold voltage in terms of fabrication parameters. [2]
- b) What is latchup? How to reduce it? [3]
- c) What are the different MOS layers? [2]
- d) Draw the layout for nMOS inverter. [3]
- e) How to choose layers? [2]
- f) What is mean by fan-in and fan-out? [3]
- g) Draw the circuit diagram of one transistor DRAM. [2]
- h) What are the advantages of serial access memories? [3]
- i) Why low power VLSI circuits are needed? [2]
- j) Compare PLAs and PALs. [3]

PART – B**(50 Marks)**

- 2.a) Explain the fabrication steps of CMOS n-well process with neat diagrams.
 - b) Identify the different regions on the V_{ds} vs. I_{ds} characteristics and explain it. [6+4]
- OR**
- 3.a) What are the different pull ups used in VLSI design? Explain them.
 - b) What will happen if logical one is applied on the BiCMOS inverter? Explain it with neat circuit diagram. [5+5]
- 4.a) Explain the process at each stage of VLSI design flow.
 - b) Draw the stick diagram for NAND gate and explain it. [5+5]
- OR**
- 5.a) What are the different design rules? Write them.
 - b) What is scaling? How to scale the different design parameters? [5+5]
- 6.a) What is dynamic logic? Explain its basic gate functionality.
 - b) How to calculate the delay due inductance in the VLSI circuits? Explain. [4+6]
- OR**
- 7.a) What are the different complex logic gates and compare their performance in all aspects.
 - b) What is wiring capacitance? How to calculate it in the design of VLSI? [5+5]

8. Design a decade counter and draw its logic and circuit diagram and also write how to improve its performance in VLSI applications? [10]

OR

9. Draw a six transistor RAM circuit and explain its working and also write its merits and demerits. [10]

- 10.a) What is FPGA and draw its structure and also write its advantages.

- b) Explain different design strategies for testing a VLSI circuit. [5+5]

OR

- 11.a) What is principle of testing CMOS circuit? Explain any one procedure for it.

- b) Design the following function using PALs:

$$Y = x'y'w + z'w' + xz$$

[5+5]

---ooOoo---