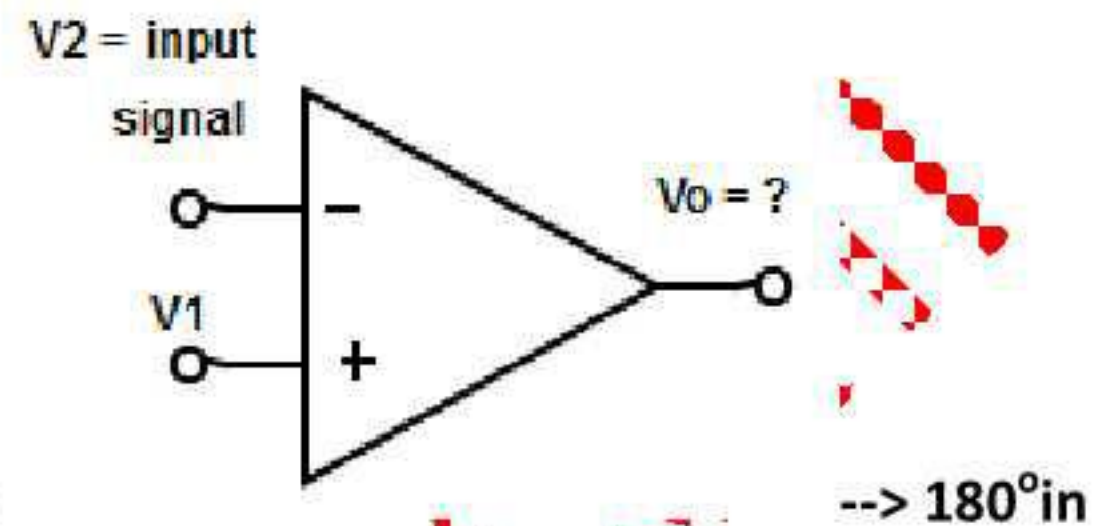


Q)Find the output voltage of an ideal op-amp. If  $V_1$  and  $V_2$  are the two input voltages-->  $V_o = A(V_1 - V_2)$

Q)How will be the output voltage obtained for an ideal op-amp?--> **Amplifies the difference between the two input voltages**

Q)An ideal op-amp requires infinite bandwidth because--> **Signals can be amplified without attenuation**

Q)Ideal op-amp has infinite voltage gain because--> **To obtain finite output voltage**



Q)Determine the output from the following circuit  
**phase with input signal**

Q)Which of the following electrical characteristics is not exhibited by an ideal op-amp?--> **Infinite output resistance**

Q)What is the purpose of differential amplifier stage in internal circuit of Op-amp?--> **Cancel common mode signal**

Q)Which of the following is not preferred for input stage of Op-amp?--> **Cascaded DC amplifier**

Q)What will be the emitter current in a differential amplifier, where both the transistor are biased and matched? (Assume current to be  $I_E = I_o/2$ )

Q)The purpose of level shifter in Op-amp internal circuit is to--> **Adjust DC voltage**

Q)How a symmetrical swing is obtained at the output of Op-amp--> **Providing amplifier with positive & negative supply voltages**


Q)Which factor determines the output voltage of an op-amp?--> **Both positive and negative saturation voltage**

Q)Which is not the internal circuit of operational amplifier?--> **Clamper**

Q)Change in value of common mode input signal in differential pair amplifier make--> **Change in voltage across collector**

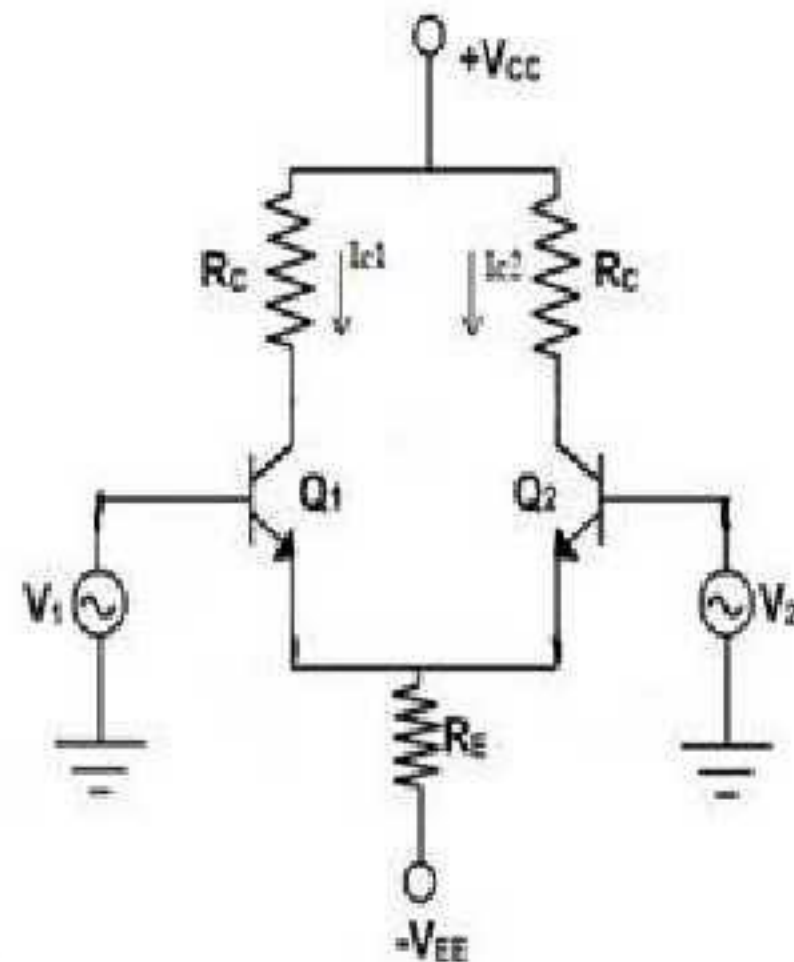Q)Find collector current  $I_{C2}$ , given input voltages are  $V_1 = 2.078\text{V}$  &  $V_2 = 2.06\text{V}$  and total current





$I_Q = 2.4\text{mA}$ . (Assume  $\alpha = 1$ )

--> **0.8Ma**

Q) At what condition differential amplifier function as a switch-->  $4V_T < V_d < -4V_T$

Q) For  $V_d > 4V_T$ , the function of differential amplifier will be--> **Limiter**

Q) Define total current ( $I_Q$ ) equation in differential amplifier with constant current bias current-->  $I_Q = 1/R_3(V_{EE}R_2/R_1 + R_2)$

Q) Constant current source in differential amplifier is also called as--> **Current Mirror**

Q) When will be the mirror effect valid-->  $\beta \gg 1$

Q) What is the purpose of diode in differential amplifier with constant current circuit?--> **Total current independent on temperature**

Q) If the value of Common Mode Rejection Ratio and Common Mode Gain are 40db and -0.12 respectively, then determine the value of differential mode gain--> **4.8**

Q) To increase the value of CMRR, which circuit is used to replace the emitter resistance  $R_E$  in differential amplifier?--> **Constant current bias**

Q) What will be the overall gain in Darlington circuit, if the individual transistor gain is 200?--> **40000**

Q) To increase the input resistance in differential amplifier, replace the transistor by--> **Darlington pair**

Q) What is the drawback in using Darlington pair in differential amplifier?--> **High offset voltage**

Q) Determine the amount of shift happens in level shifter?--> **-0.7v**

Q) A Widlar current source is used--> **to get low value of current**

Q) Determine the early voltage, if the output resistance is  $2.52\text{k}\Omega$  and input current is  $2\text{mA}$ --> **10v**


Q) In practical application of current mirror, early voltage is assumed to be--> **Infinite**

Q) The input voltage of a difference amplifier is 2.5v and 4.9v. If the transconductance is  $0.065\Omega^{-1}$ , determine the load current entering the next stage--> **0.156A**

Q) What is the need for level shifter in operational amplifier?--> **Limits the output voltage**

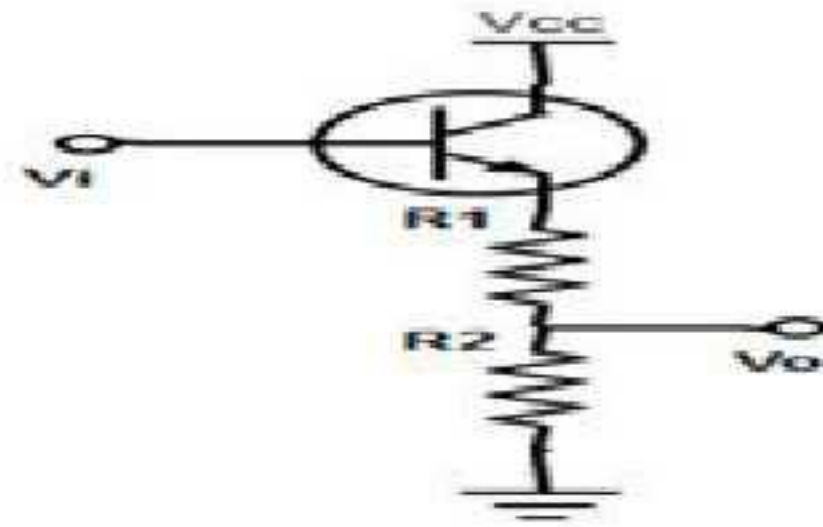Q) Limitation of an output stage amplifier, if it emitter follower with complementary transistor--> **Cross-over distortion**





Q)Find the disadvantage in the following circuit diagram:

--> **Voltage get attenuated by  $R_2$**

Q)Which circuit is used as active load for an amplifier--> **Current Mirror**

Q)What is the equation of load current for a differential amplifier with an active load?-->  $I_L = g_m V_d$

Q)introducing FET differential amplifier pair at the input stage of differential amplifier produces--> **High input resistance**

Q)Why active load is used in amplifier to obtain large gain in intermediate stage of amplifier?--> **To obtain a very large voltage gain**

Q)Compute the output voltage if the input voltage is reduced to zero in differential amplifier with one op-amp?--> **Cannot be determined**

Q)Find the value of input resistance for differential amplifier with one op-amp. If  $R_1 = R_2 = 100\Omega$  and  $R_F = R_3 = 5k\Omega$ .-->  **$R_{IFX} = 100\Omega$ ;  $R_{IFY} = 5.1k\Omega$**

Q)The bandwidth of the differential amplifier increases, if the value of--> **Closed loop voltage gain decreases**

Q)Where does the compensating network connected in an inverting amplifier.--> **Non-inverting input terminal**

Q)Why closed loop differential amplifiers are difficult to null?--> **Due to compensating network**

Q)What is the net output voltage for differential amplifier with one op-amp-->  **$V_o = -(R_F/R_1) * (V_x - V_y)$**

Q)How the value of output offset voltage is reduced in closed loop op-amp?--> **By reducing gain**

Q) $\mu A741$  is a single op-amp and available as an--> **8-pin DIP**

Q)how many IC technologies has been developed--> **2**

Q)The output voltage of an open-loop differential amplifier is equal to--> **Product of voltage gain and the difference between the two input voltages**

Q)How does the open-loop op-amp configuration classified?--> **Based on the input applied**

Q)What is the final stage in IC fabrication--> **metallization**

Q)Voltage follower is also called as--> **Non-inverting amplifier**

Q)An op-amp can be modeled as--> **voltage controlled voltage source**

Q)Compute  $R_{if}$  for an inverting amplifier with feedback, where the value of input resistance of op-amp is  $4.7k\Omega$ .-->  **$4.7k\Omega$**

Q)LSI means--> **300 to 3000 gates/chip**

Q)VLSI means--> **more than 3000gates/chip**

Q)SSI means--> **3 to30gates/chip**

Q)MSI means--> **30 to 300gates/chip**

Q)Ideal vale of  $A_v$  of IC 741 is-->  **$\infty$**

Q)Ideal vale of PIV of IC 741 is--> **0**



Q)IC 741 available in--> **8-pin**

Q)The closed loop voltage gain is reciprocal of--> **Gain of the feedback circuit**

Q)Ideal value of  $R_i$  of IC 741 is-->  $\infty$

Q)Ideal value of  $R_o$  of IC 741 is--> **0**

Q)Find the input and output voltage in voltage follower circuit?-->  $V_{in}=9v$  and  $V_{out}= 9v$

Q)Ideal value of CMRR is-->  $\infty$

Q)Op-amp block diagram contains how many difference amplifiers--> **1**

Q)If the feedback voltage and the output voltage are given as 10v and 4v. Find the gain of the feedback circuit in voltage-series feedback amplifier?--> **2.5v**

Q)How is the difference voltage calculated in closed loop non-inverting amplifier?-->  $V_{id} = V_{in} - V_f$

Q)Inverting op-amp output voltage is wrt to input--> **in phase**

Q)In non inverting terminal input output voltages--> **180**

Q)In which configuration does the op-amp function as a high gain amplifier?--> **All of the mentioned**

Q)What is the purpose of differential amplifier stage in internal circuit of Op-amp?--> **Cancel common mode signal**

Q)Sine wave is converted into square wave which application of op-amp is--> **Schmitt trigger**

Q)How a symmetrical swing is obtained at the output of Op-amp--> **Providing amplifier with positive & negative voltage**

Q)The differential amplifier output voltage is-->  $V_o - V_i$

Q)The three input summer output voltage of IC 741 is-->  $v_0 + v_1 + v_2$

Q)Which is not the internal circuit of operational amplifier?--> **Clamper**

Q)The purpose of level shifter in Op-amp internal circuit is to--> **Adjust DC voltage**

$$V_o = - \left( \frac{R_f}{R_2} V_2 - \frac{R_f}{R_3} \frac{R_f}{R_1} V_1 \right) \rightarrow$$

Q)How many op-amps are required to implement this equation?

**2**

Q)How many op-amps are required to implement this

$$V_o = \frac{R_3}{R_1 + R_3} \frac{R_2 + R_4}{R_2} V_1 - \frac{R_4}{R_2} V_2 \rightarrow 1$$

equation?

Q)Full wave rectifier PIV voltage is--> **2V<sub>m</sub>**

Q)In op-amp will act as an integrator which elements are present--> **resistor**

Q)IC 741 op-amp is which type package--> **DIP**


Q)MSI means--> **30 to 300 gates/chip**

Q)LSI means--> **300 to 3000 gates/chip**

Q)How many op-amps are required to implement this

$$V_o = \frac{R_3}{R_1 + R_3} \frac{R_2 + R_4}{R_2} V_1 - \frac{R_4}{R_2} V_2 \rightarrow 1$$

equation?

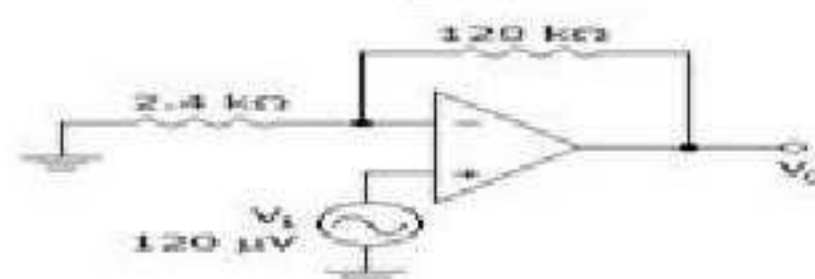


Q)Calculate the output voltage.

--> **6.12mv**



## Day2 Linear IC Applications ECE

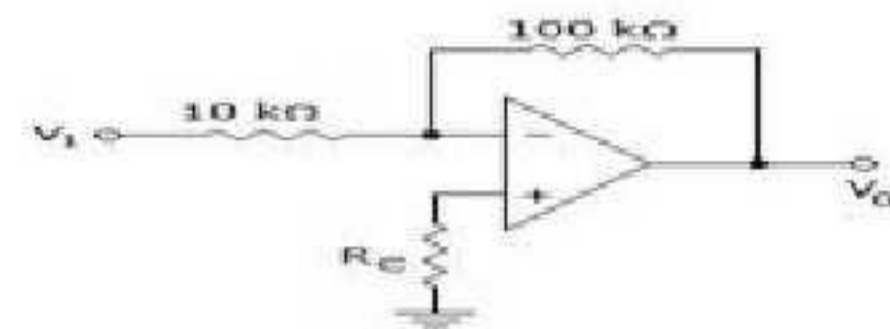

Q) Calculate the input voltage for this circuit if  $V_o = 11$  V.

**1.1v**

Q) An example of an instrumentation circuit is a(n) \_\_\_\_\_. --> **All of the above**

Q) How many op-amps are required to implement this


$$V_o = - \left( \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

equation?

--> **1**

Q) A comparator is an example of a(n) --> **nonlinear circuit**

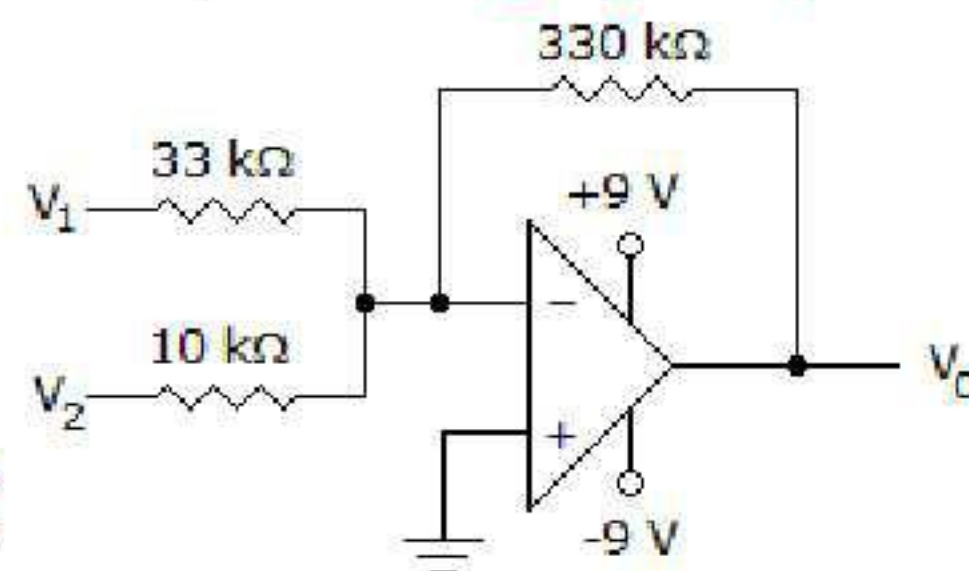
Q) In an averaging amplifier, the input resistances are --> **greater than the feedback resistance**



Q) Calculate the output voltage if  $V_1 = V_2 = 0.15$  V.

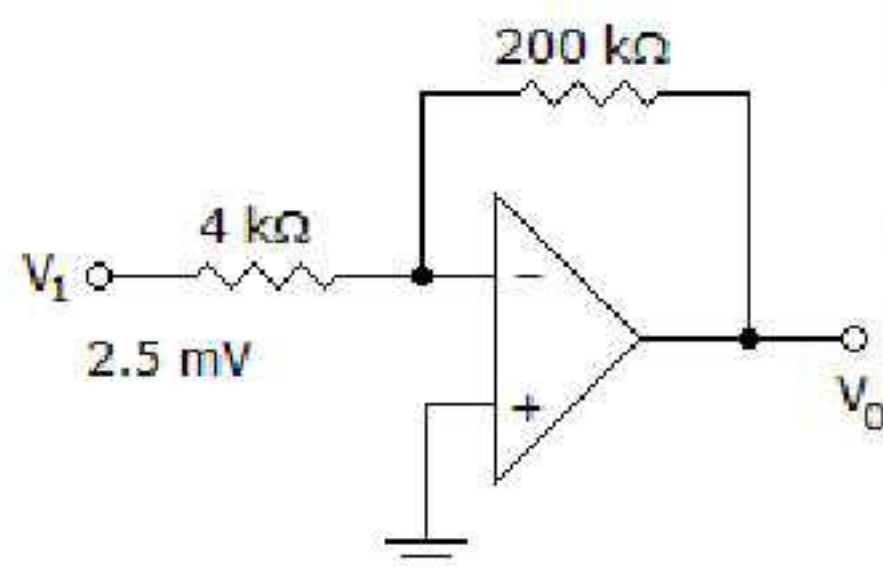**6.45V**

Q) Determine the output voltage for this circuit with a sinusoidal input of 2.5




Mv

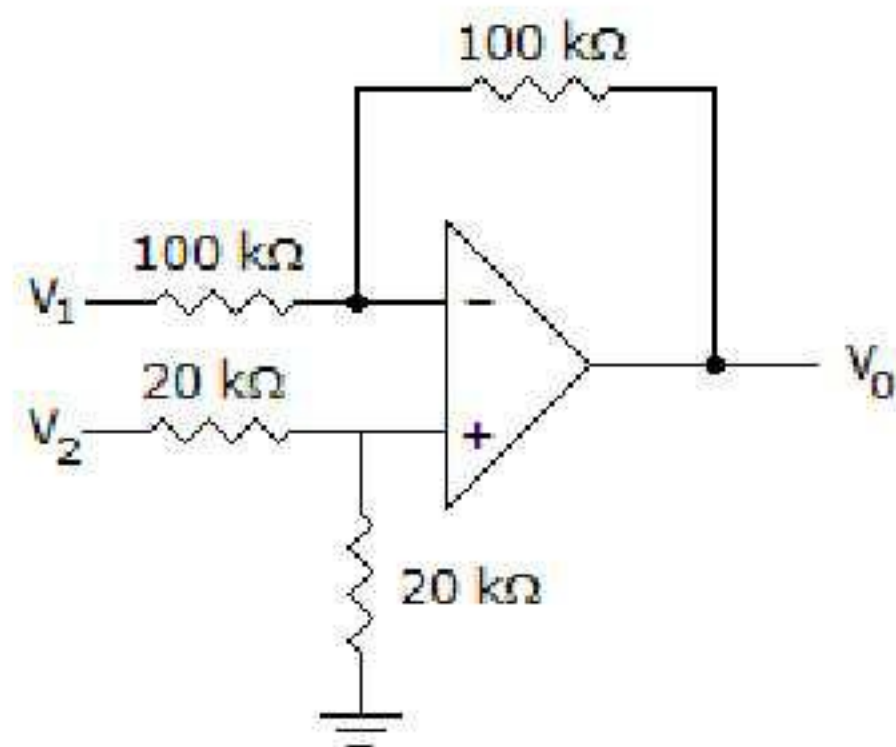--> **-0.125V**

Q) How many op-amps are required to implement this equation?  $V_o = V_1$  --> **1**






Q) Determine the output voltage when  $V_1 = V_2 = 1$  V.

Q) A digital-to-analog converter is an application of the--> **scaling adder**

--> 0v

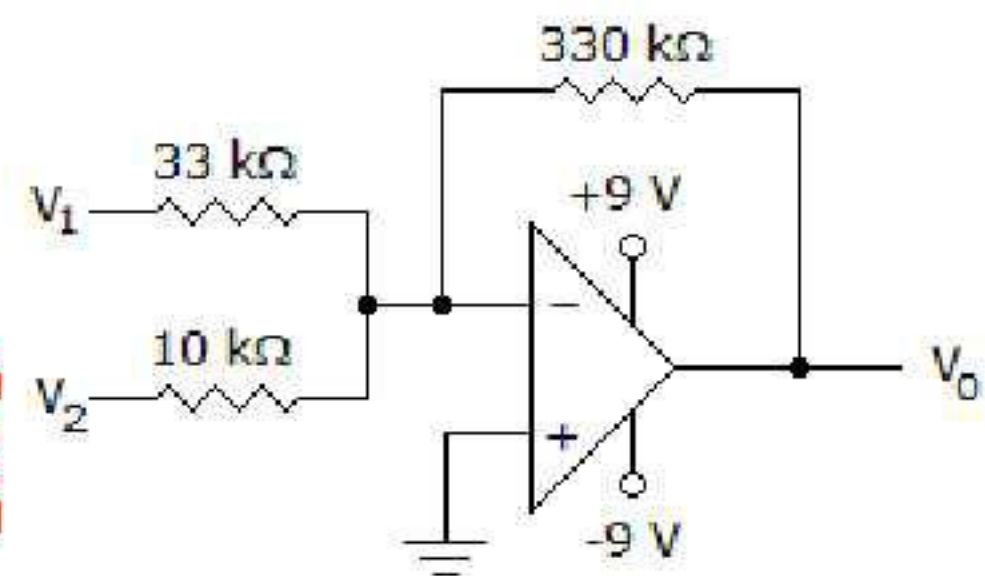


Q) Calculate the output voltage if  $V_1 = 0.2$  V and  $V_2 = 0$  V.

--> 2v

Q) A basic series regulator has--> **both an error detector and a reference voltage**

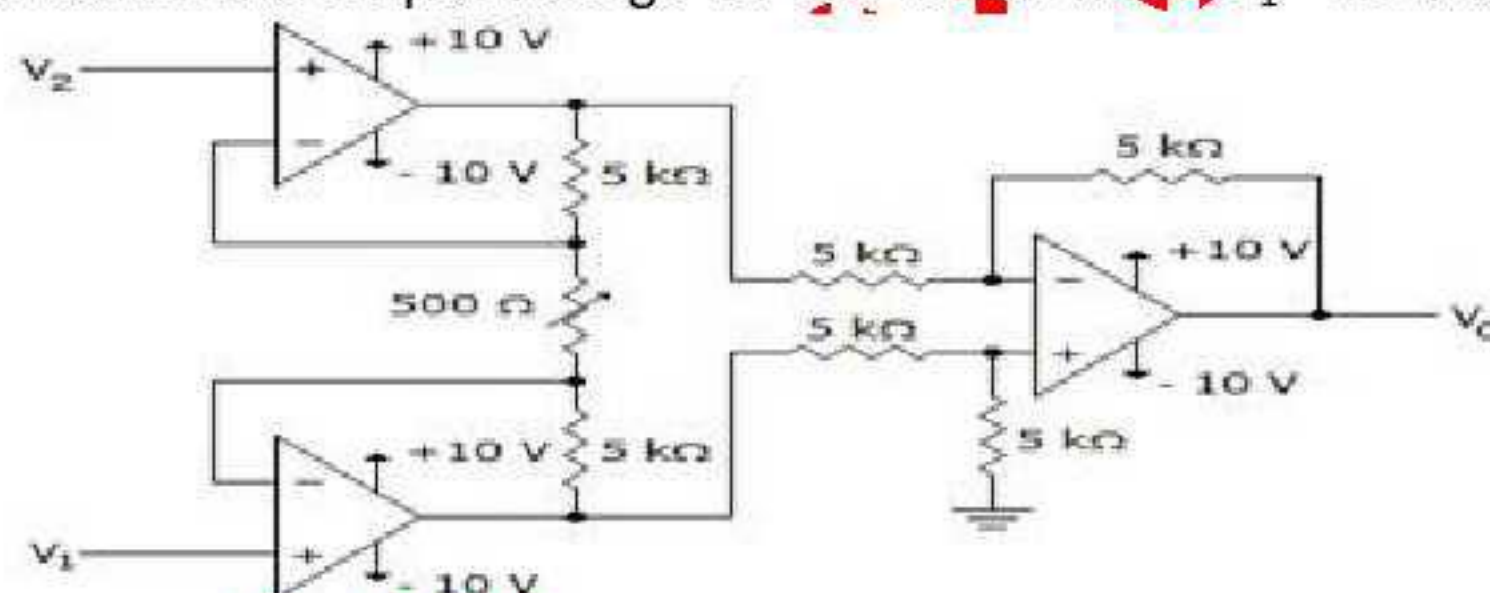Q) Calculate the output voltage for this circuit when  $V_1 = 2.5$  V and  $V_2 = 2.25$



V.

--> 5.25V

Q) The ramp voltage at the output of an op-amp integrator--> **increases or decreases at a linear rate**

Q) Circuits that shift the dc level of a signal are called--> **clampers**


Q) Why open-loop op-amp configurations are not used in linear applications?--> **Output switches between positive and negative saturation**

Q) What happens if any positive input signal is applied to open-loop configuration?--> **Output reaches saturation level**

Q) A zero-level detector is a--> **comparator with a trip point referenced to zero**

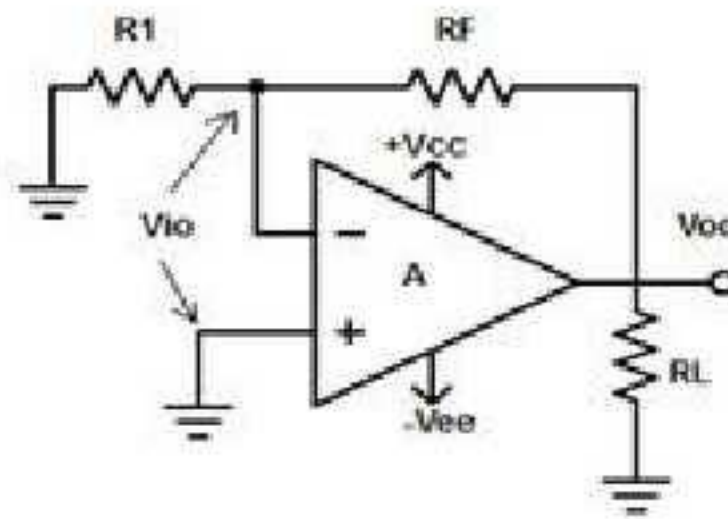Q) For the feedback circuit of voltage series feedback amplifier, find the feedback voltage for the specifications:  $R_1 = 1$  kΩ,  $R_F = 10$  kΩ and  $V_0 = 25$  v--> **2.3v**





Q)What happens if  $R_1 \gg R_f$  in the circuit  
**output offset voltage is present**

--> **Some amount of**

Q)Which factor determines the gain of the voltage series feedback amplifier?--> **Ratio of two resistors**

Q)If the feedback voltage and the output voltage are given as 10v and 4v. Find the gain of the feedback circuit in voltage-series feedback amplifier?--> **2.5v**

Q)How is the difference voltage calculated in closed loop non-inverting amplifier?-->  **$V_{id} = V_{in} - V_f$**

Q)Why the feedback circuit is said to be negative for voltage series feedback amplifier?-->

**Feedback voltage is  $180^\circ$  out of phase with respect to input voltage.**

Q)What is the net output voltage for differential amplifier with one op-amp-->  **$V_o = -(R_f/R_1) * (V_x - V_y)$**

Q)Determine the output resistance of differential amplifier with three op-amp. The op-amp used is 741c, with  $A=200000$  and  $R_o$ . The output and difference of input voltages are 44 and 11.-  
 --> **1.5m $\Omega$**

Q)The characteristics of non-inverting amplifier is identical to--> **Differential Amplifier with two op-amp**

Q)Why differential amplifiers are preferred for instrumentation and industrial applications?-->  
**Reject common mode voltage**

Q)Which of the following is a combination of inverting and non-inverting amplifier?-->  
**Differential amplifier with one op-amp**

Q)What will be the output voltage when  $V_x=0v$ ? (Where  $V_x$  > inverting input terminal of differential amplifier with one op-amp)-->  **$V_o = (1 + R_f/R_1) * V_1$**

Q)The difference between the input and output voltage are -1v and 17v. Calculate the closed loop voltage gain of differential amplifier with one op-amp?--> **-17**

Q)The gain of differential amplifier with one op-amp is same as that of--> **The inverting amplifier**

Q)In which configuration does the op-amp function as a high gain amplifier?--> **All of the mentioned**

Q)When the non-inverting input terminal of an op-amp is equal to that of the inverting input terminal--> **All of the mentioned**

Q)The bandwidth of a non-inverting amplifier with feedback is equal to--> **c)  $f_o(1+A)$**

Q)When the input voltage is reduced to zero in a closed loop configuration the circuit acts as-->  
**Inverting and non-inverting amplifier**

Q)The closed loop voltage gain is reciprocal of--> **Gain of the feedback circuit**