

**I B. Tech II Semester Supplementary Examinations, July/August 2021**  
**NETWORK ANALYSIS**  
 (Com. to ECE, EIE, E Com E)

Time: 3 hours

Max. Marks: 70


- Note: 1. Question paper consists of two parts (**Part-A** and **Part-B**)  
 2. Answering the question in **Part-A** is Compulsory  
 3. Answer any **THREE** Questions from **Part-B**

**PART -A**

1. a) What are the different types of dependent sources, describe briefly? (4M)
- b) Given  $i(t) = 5 \cos (500t - 120^\circ)$  A, determine the period of the current and the frequency in Hertz. (3M)
- c) What is meant by resonant frequency of RLC series circuit? (3M)
- d) Describe briefly Milliman's theorem with an example. (4M)
- e) Compare the y-parameter equations with the node-voltage equations and verify that the z and y matrices are the inverse of one another. (4M)
- f) Obtain the natural response of RL series circuit. (4M)

**PART -B**

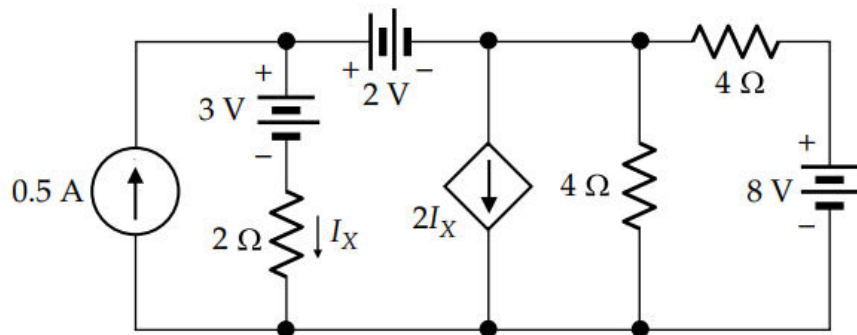
2. a) By using the nodal analysis determine all node voltages and current,  $I_X$  of the circuit shown in figure. (6M)



Figure


- b) Given  $\mathbf{A} = 3 + j5$ ,  $\mathbf{B} = 10 - j8$ , and  $\mathbf{C} = j12$ , determine the phasors resulting from the following operations: (i)  $\mathbf{ABC}$ , (ii)  $(\mathbf{A/B})\mathbf{C}$  (iii)  $\mathbf{A/B/C}$   
Express the result in rectangular and polar forms. (5M)
- c) How do you obtain cut set matrix, describe with an example? (5M)

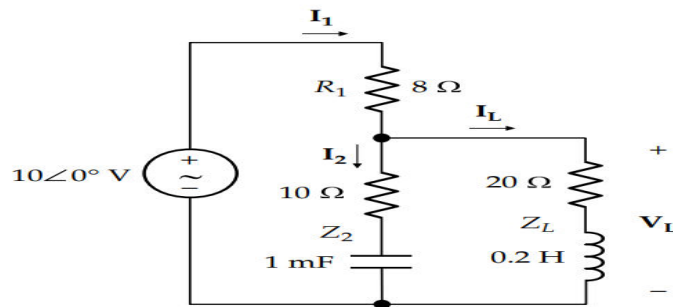3. a) Given the circuit of figure, determine  $V_L$ ,  $I_L$ ,  $I_1$ , and  $I_2$ , assuming that  $\omega = 100$  rad/s. (6M)




Figure

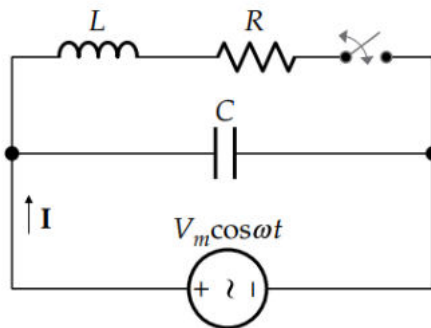- b) The current,  $I$  remains the same of the circuit as shown in the figure irrespective of whether the switch is open or closed. Show that under these conditions  $2\omega^2 LC = 1$ . (5M)



Figure

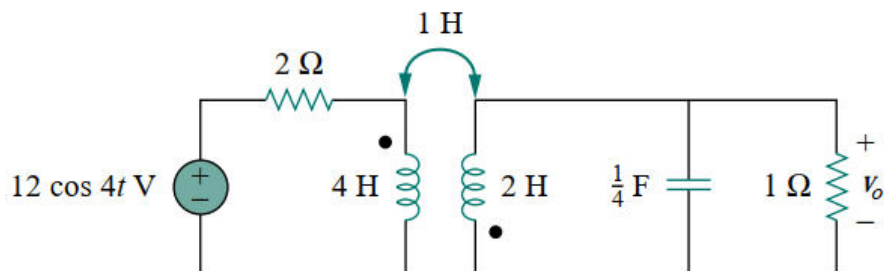
- c) A capacitor of impedance  $Z_C$  is connected in parallel with a load of  $(300 + j450)$  Ω. Determine  $Z_C$  so that the equivalent load is purely resistive. (5M)
4. a) In the circuit of figure, (i) find the coupling coefficient, (ii) Calculate  $V_o$ , (iii) determine the energy stored in the coupled inductors at  $t = 2$  s. (8M)



Figure


- b) A series  $RLC$  network has  $R = 2$  kΩ,  $L = 40$  mH, and  $C = 1$  μF. Calculate the impedance at resonance and at one-fourth, one-half, and twice, the resonant frequency. (8M)

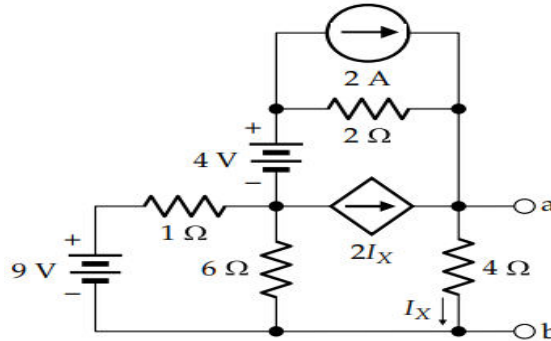5. a) Derive Thevenin's Equivalent Circuit looking into terminals 'ab' as shown in the figure, (i) keeping the  $6\ \Omega$  resistor in place, (ii) temporarily removing this resistor. (8M)




Figure

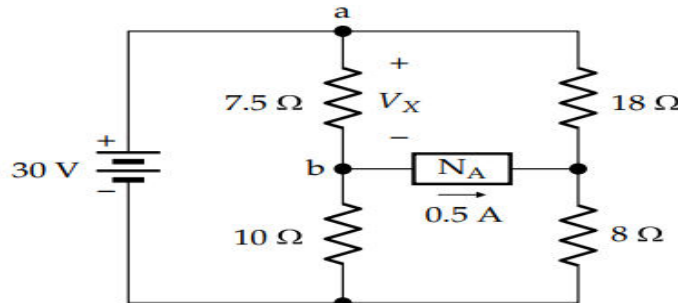- b) Determine  $V_X$  in figure by using the substitution theorem between nodes 'ab', (8M) where ' $N_A$ ' is an unspecified circuit that passes a current of 0.5 A.




Figure

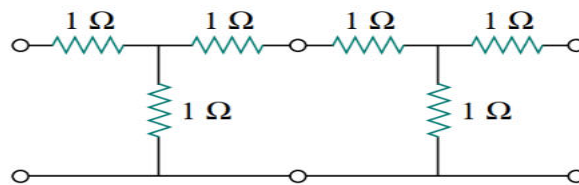6. a) Determine the ABCD parameters of the circuit in figure, by partition the circuit into sub-circuit and cascade them? (8M)




Figure

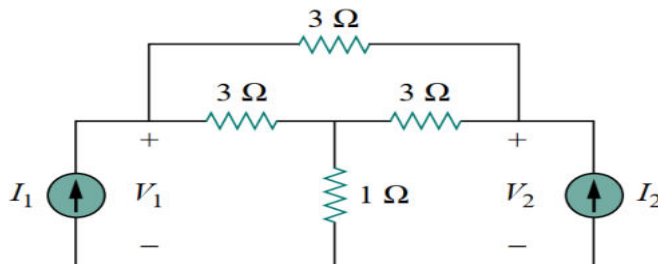- b) In the bridge circuit of figure,  $I_1 = 10\ \text{A}$  and  $I_2 = -4\ \text{A}$ . (i) Find  $V_1$  and  $V_2$  using y (8M) parameters. (ii) Confirm the results in part (i) by direct circuit analysis.




Figure

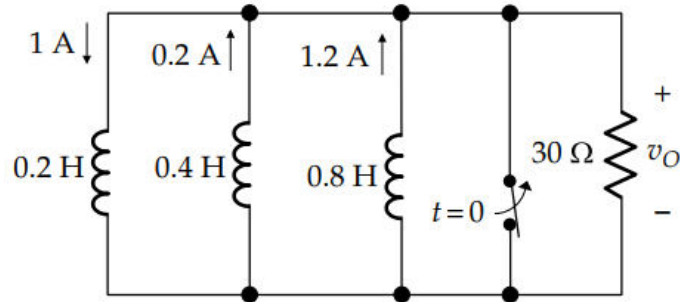7. a) The three inductors in figure have the initial currents shown. The switch is opened at  $t = 0$ . Determine  $v_o(t)$  for  $t > 0$  and the final currents in the inductors. (8M)



Figure

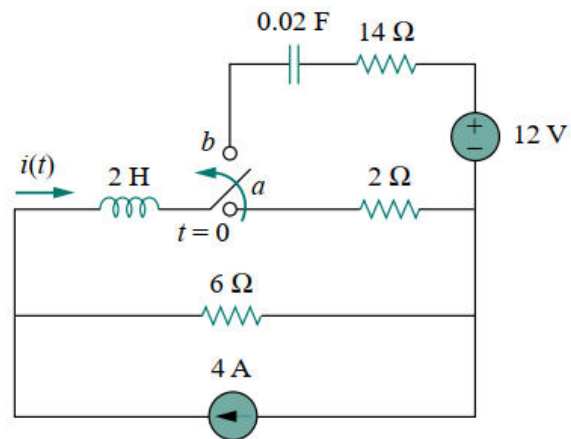- b) The switch in the circuit of figure is moved from position  $a$  to  $b$  at  $t = 0$ . Determine  $i(t)$  for  $t > 0$ . (8M)



Figure