

I B. Tech II Semester Supplementary Examinations, November - 2021

NETWORK ANALYSIS

(Com. to ECE, EIE, E Com E)

Time: 3 hours

Max. Marks: 70


- Note: 1. Question paper consists of two parts (**Part-A** and **Part-B**)
 2. Answering the question in **Part-A** is Compulsory
 3. Answer any **THREE** Questions from **Part-B**

PART -A

1. a) What is the difference between active and passive element? (3M)
- b) Given $v(t) = 20 \cos(\omega t - 45^\circ)$ V and $i(t) = 10 \sin(\omega t - 80^\circ)$ A, determine which variable leads the other and by what angle. (3M)
- c) How do you use dot convention for ideal transformer circuit? (4M)
- d) Describe briefly Reciprocity theorem with an example? (4M)
- e) Define h-parameters? How do you obtain inverse h-parameters? (4M)
- f) Obtain the natural response of RC series circuit? (4M)


PART -B

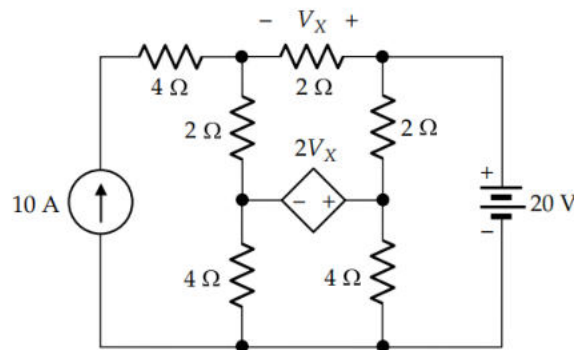2. a) By using the mesh analysis determine all branch currents and voltage, V_X of the circuit shown in figure. (8M)




Figure

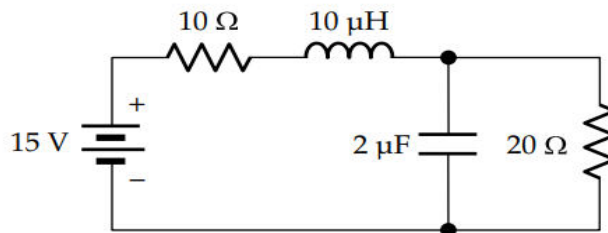- b) (i) Derive the dual of the circuit of figure, (ii) represent the two circuits in the dc steady state; (iii) compare voltage division in the given circuit with current division in the dual circuit; (iv) compare the power delivered or absorbed by each circuit element in the two circuits. (8M)



Figure

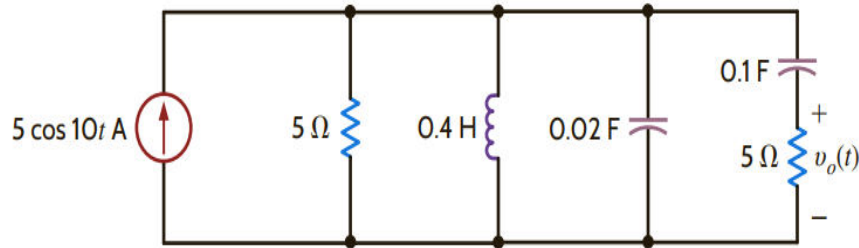3. a) In the circuit shown in the figure, Find $v_o(t)$. (8M)




Figure

- b) For each of the following cases, find the complex power, the average power, and the reactive power: (8M)


- (i) $v(t) = 112 \cos(\omega t + 10^\circ)$ V, $i(t) = 4 \cos(\omega t - 50^\circ)$ A
 (ii) $v(t) = 160 \cos 377t$ V, $i(t) = 4 \cos(377t + 45^\circ)$ A
 (iii) $V = 80 \angle 60^\circ$ V rms, $Z = 50 \angle 30^\circ \Omega$ (iv) $I = 10 \angle 60^\circ$ V rms, $Z = 100 \angle 45^\circ \Omega$

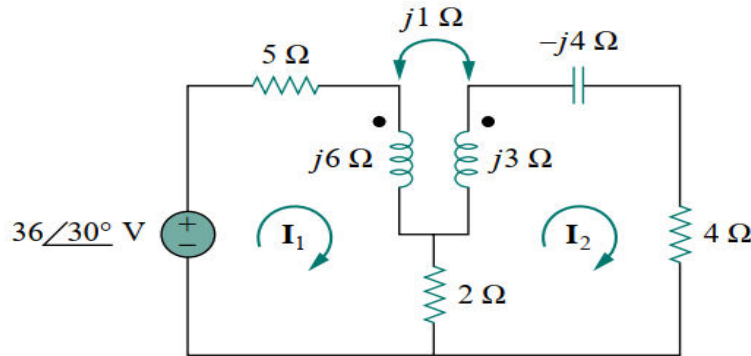4. a) Find I_1 and I_2 in the circuit of below figure. Calculate the power absorbed by the 4 Ω resistor. (8M)




Figure

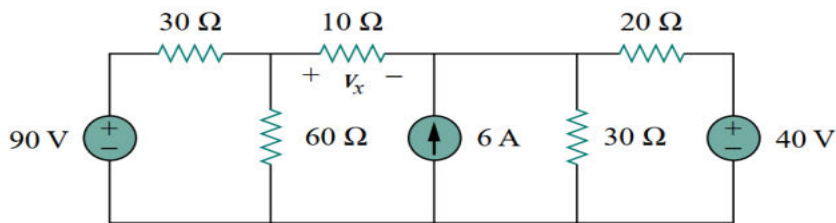- b) It is expected that a parallel RLC resonant circuit has a mid-band admittance of 25×10^3 S, quality factor of 80, and a resonant frequency of 200 krad/s. Calculate the values of R , L , and C . Find the bandwidth and the half-power frequencies. (8M)
5. a) Use superposition to obtain V_x in the circuit shown in figure. (8M)




Figure

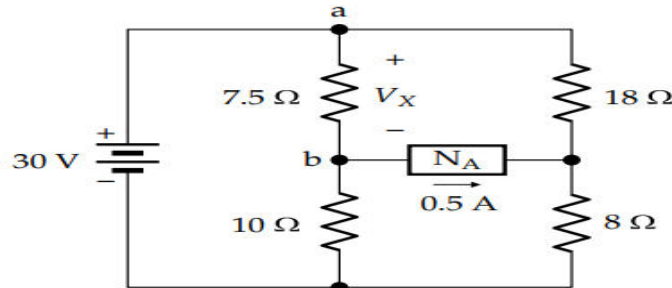- b) Determine V_X and maximum power transfer across the terminals 'ab', as shown in the figure, by deriving thevenin's equivalent circuit, where ' N_A ' in the circuit that passes a current of 0.5 A. (8M)




Figure

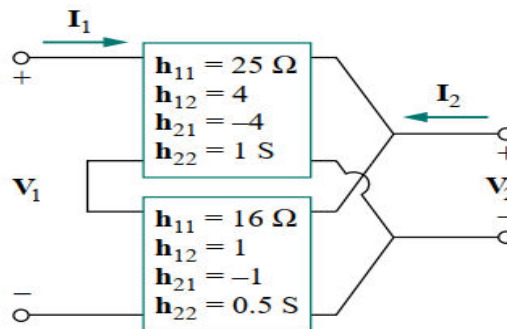6. a) For a two-port, let $A = 4$, $B = 30$, $C = 0.1$ S, and $D = 1.5$. Calculate the input impedance $Z_{in} = V_1/I_1$, when, (i) the output terminals are short-circuited, (ii) the output port is open-circuited, (iii) the output port is terminated by a 10-Ω load. (8M)
- b) A series-parallel connection of two two-ports is shown in figure. Determine the zparameter representation of the network. (8M)




Figure

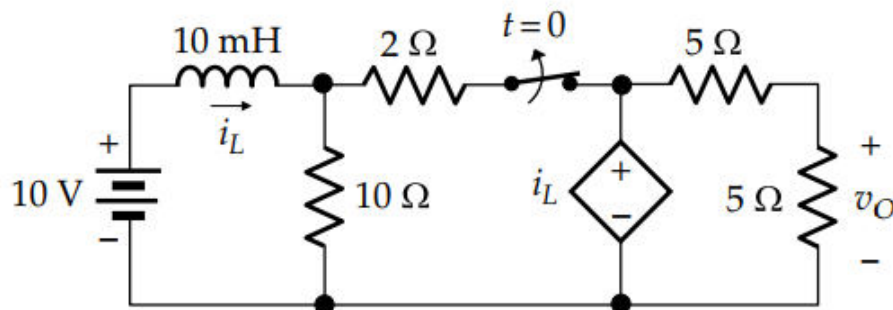7. a) The switch in figure is opened at $t = 0$ after being closed for a long time. Determine $I_L(0+)$ and $v_o(t)$. (8M)



Figure

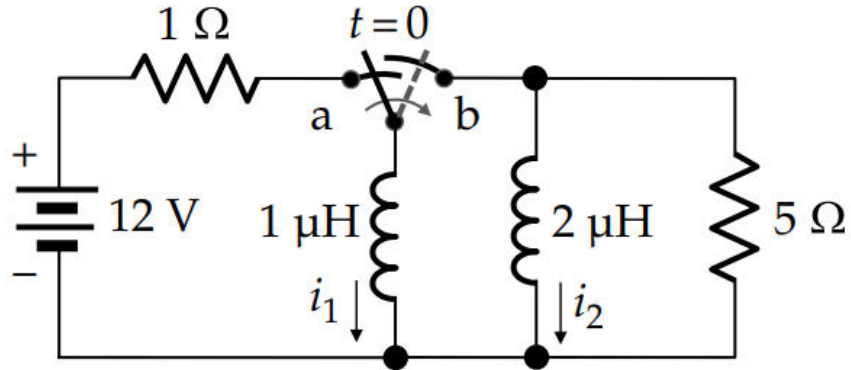- b) The switch in figure is moved to position 'b' at $t = 0$ after being in position 'a' for a long time. Determine the final values of i_1 and i_2 (8M)



Figure