

Question Paper Consists of **Part-A** and **Part-B**
 Answering the question in **Part-A** is Compulsory,
Three Questions should be answered from **Part-B**

PART-A

1. (a) What is meant by Unilateral and bi-lateral element?
- (b) Explain how voltage source with a source resistance can be converted into an equivalent current source.
- (c) Distinguish between steady state and transient response.
- (d) Define mutual inductance and self inductance
- (e) State Maximum power transfer theorem.
- (f) Mention the Properties of a series RLC circuit.
- (g) Define time constant of RC circuit.

[3+3+4+3+3+3+3]

PART -B

2. (a) Draw the graph of the network given in Figure 1, find tie test schedule and determine loop currents.

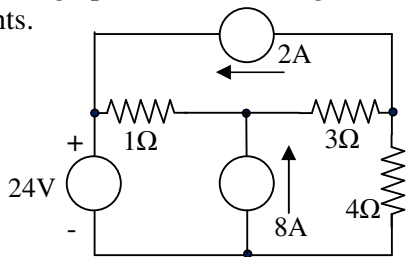


Figure 1

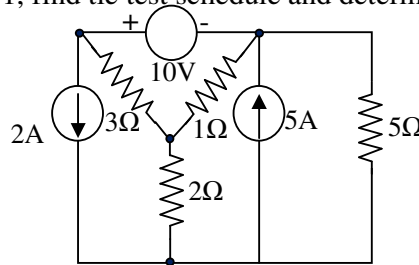


Figure 2

- (b) Find the power delivered by the 5A current source (in Figure 2) using nodal analysis. [8+8]

3. (a) Find v_x in the network of Figure 3, if the current through $2 + j3$ element is zero.

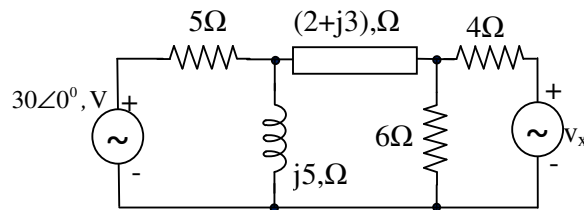


Figure 3

- (b) A sinusoidal voltage $25\sin 10t$ is applied at time $t=0$ to a series R-L circuit having $R=5\Omega$ and $L=1H$ Find $i(t)$ and sketch it. Assume Zero current through the inductor before applying the voltage. [8+8]



4. (a) For the circuit shown in below Figure 4, find the value of ω so that current and source emf are in phase. Also find the current at this frequency.

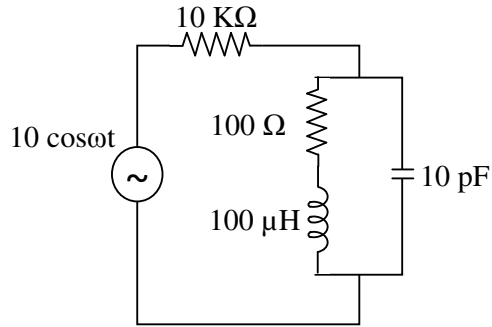


Figure 4

- (b) Two identical coils with $L=0.02\text{H}$ have a coefficient of coupling of 0.8. Find mutual inductance and the two equivalent inductances with the two coils connected in series aiding and series opposing. Derive the equations employed. [8+8]
5. (a) Compute the current in 23 ohm resistor using super position theorem for the circuit shown in Figure 5.

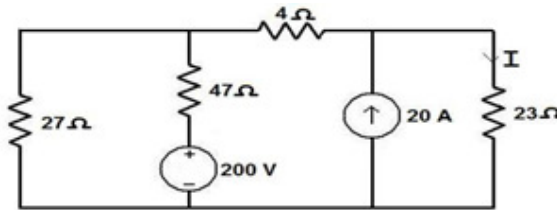


Figure.5

- (b) Find the value of R_L so that maximum power is delivered to the load resistance shown in below Figure 6. [8+8]

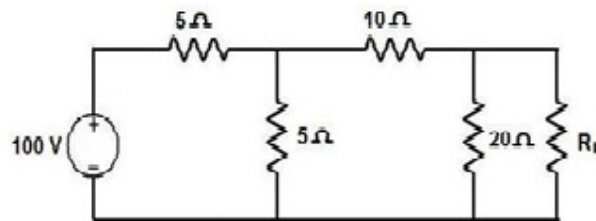


Figure.6



6. a) Given the ABCD parameters of a two-port network, determine its z-parameters. [8]
 b) Find the y-parameters for the network given in Figure.7 [8]

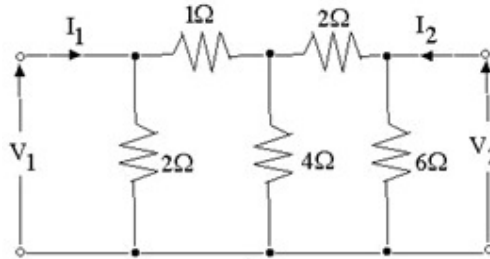


Figure.7

7. (a) The circuit (Figure 8) shown, the switch position changes from 1 to 2 at $t=0$. Determine the initial conditions i , di/dt , d^2i/dt^2 at $t=0^+$ [8]

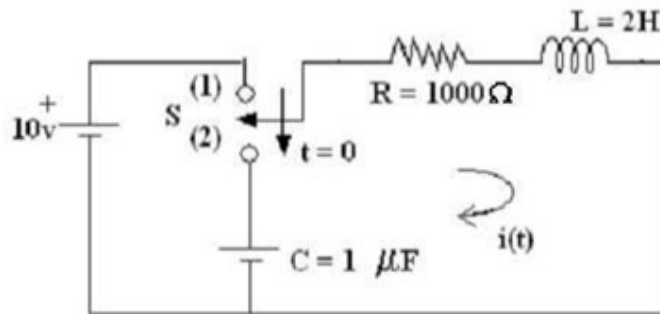


Figure.8

- (b) For the circuit shown in figure.9, find the voltage across the resistor 0.5 ohm when the switch, S is opened at $t=0$. Assume that there is no charge on the capacitor and no current in the inductor before switching. [8]

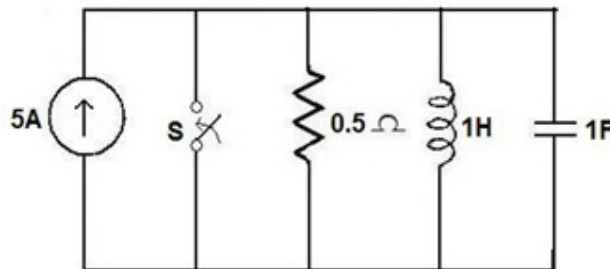


Figure.9

