

I B. Tech II Semester Supplementary Examinations, March - 2022
NETWORK ANALYSIS
 (Com. to ECE, EIE)


Time: 3 hours

Max. Marks: 75

Answer any five Questions one Question from Each Unit
All Questions Carry Equal Marks


Unit - I

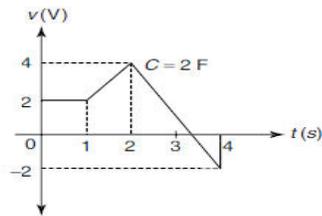1. a) Explain the need for Source transformation and also give its uses (7M)
- b) The following voltage shown in the figure is applied to the capacitor of 2F. Draw its current waveform: (8M)




Or

2. a) Explain the following w.r.t Graph Theory: (8M)
- | | | | |
|--------------------|-----------------------|------------------|-----------------|
| i) Planar graph | ii) Non- planar Graph | iii) Sub – graph | iv) Path |
| v) Connected graph | vi) Rank of a Graph | vii) Tree | viii) co - tree |
- b) Find the currents I_x and I_y for the following circuit: (7M)

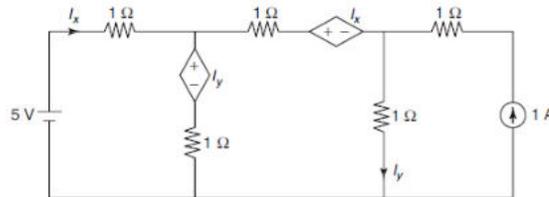


Unit - II

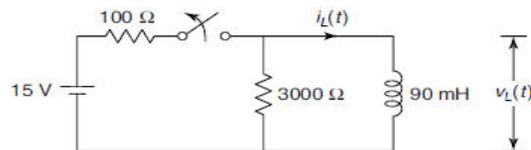3. For the network shown below, a steady state is reached with the switch closed. The switch is opened at $t = 0$. Obtain expressions for $i_L(t)$ and $v_L(t)$ (15M)




Or

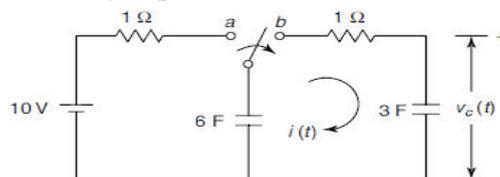4. a) Explain the salient points of the Series RLC circuit when excited by a DC Source with the corresponding current responses of it. (8M)
- b) For the following network, the switch is moved from a to b at $t = 0$. Determine $i(t)$ and $v_C(t)$ using Laplace transform method. (7M)




Unit - III

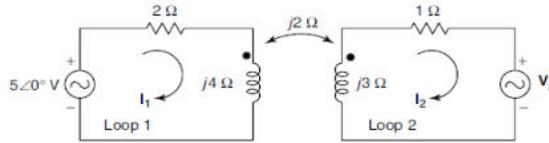5. a) Derive the Effective inductance for a differential coupling connected two coils L_1 and L_2 connected in series with the coefficient of mutual inductance 'M'. (7M)
- b) Find the voltage V_2 in the circuit shown such that the current in the loop1 is zero. (8M)




Or

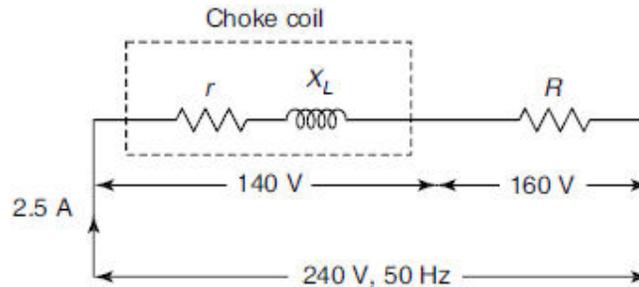6. A choke coil is connected in series with fixed resistor as shown in Figure below. A 240 V, 50 Hz supply is applied and a current of 2.5 A flows. If the voltage drops across the coil and fixed resistor are 140 V and 160 V respectively, calculate the value of the fixed resistance, the resistance and inductance of the coil, and power drawn by the coil. (15M)



Unit - IV

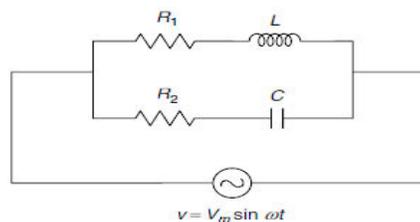7. a) Derive the expression for the resonant frequency of the parallel circuit shown in the figure below: (8M)




- b) A resistor and a capacitor are connected in series with a variable inductor. When the circuit is connected to a 230 V, 50 Hz supply, the maximum current obtained by varying the inductance is 2 A. The voltage across the capacitor is 500 V. Calculate the resistance, inductance and capacitance of the circuit. (7M)

Or


8. a) State and explain Tellegen's theorem (5M)

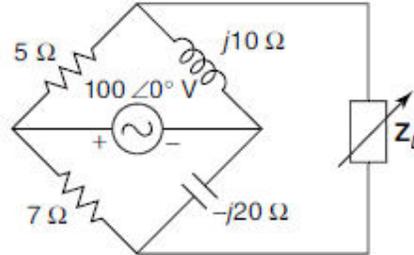- b) Find the value of Z_L for maximum power transfer in the network shown below and find maximum power. (10M)



Unit - V

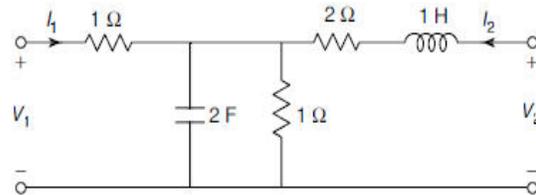9. Find Z – parameter for the following network: (15M)



Or

10. a) Explain the rules to be satisfied for cascading of two port networks (5M)
- b) The Z-parameters of a two-port network are $Z_{11} = 2.1 \Omega$, $Z_{12} = Z_{21} = 0.6 \Omega$, $Z_{22} = 1.6 \Omega$. A resistor of 2Ω is connected across port 2. What voltage must be applied at port 1 to produce a current of 0.5 A in the 2Ω resistor. (10M)